

IC (Integrated circuit)

IC is a miniature low cost electronics circuit consisting of active and passive components that are irreparably joined together on a single digital chip of silicon.

Advantages of IC

1. Miniaturization and hence increased equipment density
2. Cost reduction due to batch processing when IC is produced in large quantity cost is less reduced
3. Increased system reliability due to elimination of soldered joints.
4. Improve functional performance
5. Matched device
6. Increased operating speed.
7. Reduction in power consumption

Classification of ICs

On the basis of application ICs are classified ~~as~~ as -

- i) Digital IC
- ii) Analog IC
- iii) Mixed signal IC

Digital IC → ex → AND gate, NOT gate, OR gate and all other gates, registers, counters, timers etc.


They deal with the digital data i.e. receive digital data as input as well as provide digital data as output. Digital IC require digital input and output, power supply and input/output pins.

Analog IC → Amplifier, filter, modulators, Op-Amp (widely used)

These ICs are also known as linear ICs because the output of the circuit has a linear relation with the input of the circuit.

In analog ICs, we use external components for setting or adjusting the operating point (gain also in some cases) of the circuit.


analog input and analog output

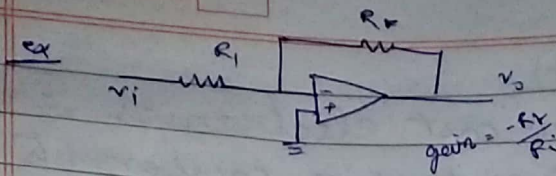


In this circuit resistors are used to set the gain of the circuit.

Mixed signal IC

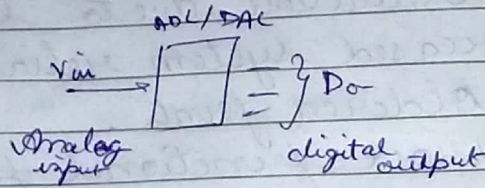They are easy to design but should be interference free. They contain both circuits digital as well as analog circuits on the same IC. They are designed for special purpose $ex \rightarrow$ ADC and DAC.



ii) On the basis of technology.

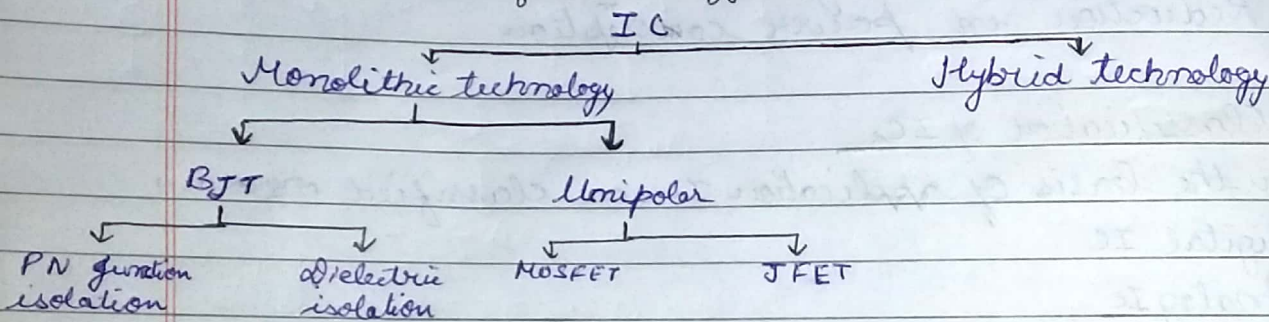


Monolithic technology

In monolithic technology, all the circuit components both active and passive and their interconnections are manufactured into or on top of the single chip of silicon.

Hybrid technology

In hybrid, components are manufactured and then they are interconnected either through metallization or wire bonds but it is suitable only for small circuits.

MC 3/1/17
 in KB only

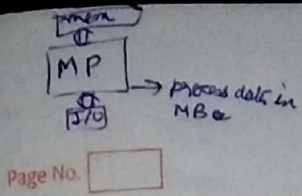

MP is used during data
 PL is " only for small data

AVR format → ARM processor

ARM → advanced
 risc machine

ARM → use core (processing unit)
 → reduced instruction set computer

Date: ___/___/___

ii) On the basis of level of integration

SSI (small scale integration) < 10 transistor
 In this ICs are manufactured with less than 10 transistor

MSI (medium scale integration) < 100

LSI (large scale integration) < 1000

VLSI (very large scale integration) > 1000

ULSI (ultra large scale integration)

WSI (wafer scale integration)


Specialty designed for super computers.
 special case of VLSI/ULSI in which we work of wafers instead of chip

first IC manufacturer
 using VLSI technology
 is Intel 1MB (one million
 transistors)
 RAM
 in 1985

SOC (System on chip) all the features required for the operation of systems to design
 IC are fabricated on the single chip then this chip
 is known as SOC.

To reduce the size of IC
 3D-IC wafer is either connected vertically as well as horizontally
 ea → 2D and PCB

The basic building blocks of an op-amp

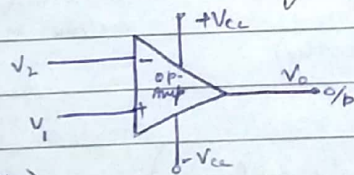


$V_o = A(V_1 - V_2)$

Ideal characteristics
 input imp. → ∞
 output imp. → 0
 gain → ∞


If we look inside an op-amp there are 4 stages →
 differential amp, gain (amp having high gain), Buffer, Bias (which provide

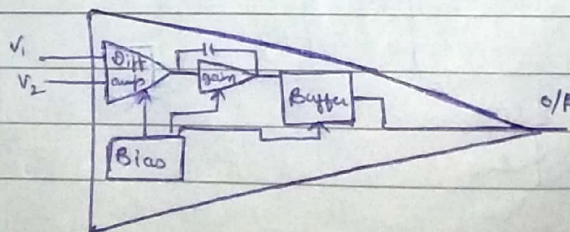const voltage to sub unit of op-amp.
 in supply may fluctuate } these should be compensated
 temp change } or avoided
 (atmospheric temp change
 (self heating of the electronic component)



RS - Source Resistance

Differential amplifier

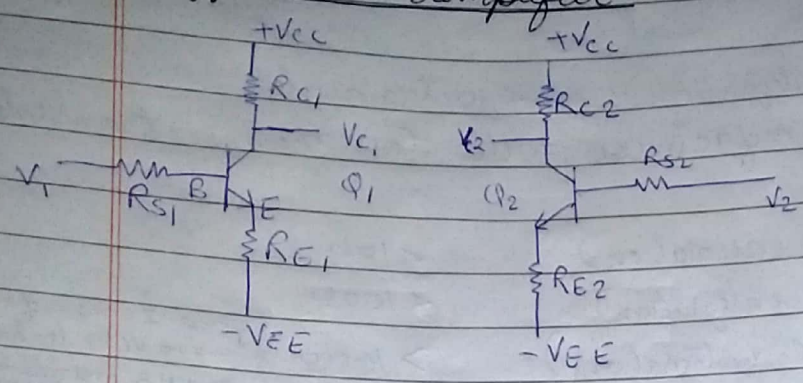

$$R_{C1} = R_{C2} = R_C$$


$$R_{E1} = R_{E2} = R_E$$

$$R_{S1} = R_{S2} = R_S$$

$$I_{C1} = I_{C2} = I_C$$

$$I_{B1} = I_{B2} = I_B$$

$$I_{E1} = I_{E2} = I_E$$

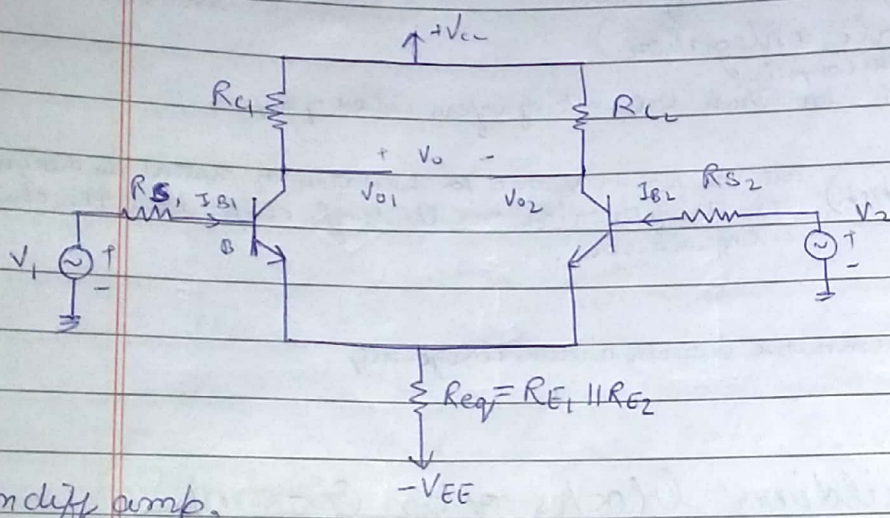

$$V_o = V_{o1} - V_{o2}$$

$$V_{o1} = A V_1$$

$$V_{o2} = A V_2$$

$$V_o = A(V_1 - V_2)$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B$$

$$V_C = V_{CC} - I_C R_C$$

This op amplifier amplifies the diff of 2 voltages not the two voltage simultaneously - that's why it is called diff amplifier


In diff amp,

Noise ~~also~~ gets reduced.
(due to its diff amplification noise gets cancelled)

+ Two input and one output, and output is taken across two terminals

DC analysis (zero voltage analysis)

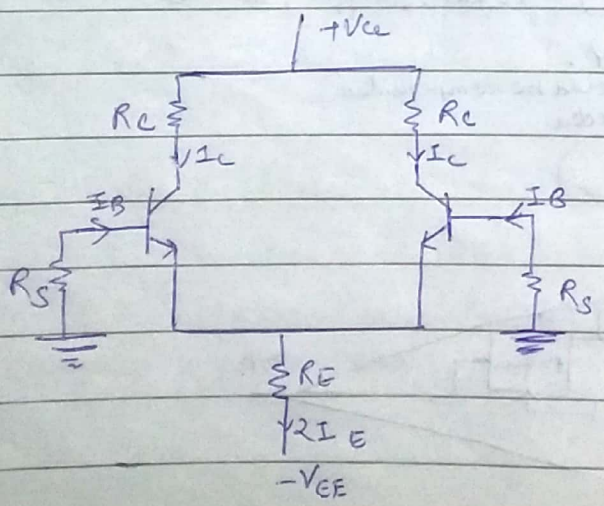operating points $\rightarrow I_{CQ}, V_{CEQ}$



R_s - Source Resistance

Page No.

Date / /

$$I_B R_s + V_{BE} + 2I_E R_E - V_{EE} = 0 \quad \text{--- (1)}$$

$$I_C = \beta I_B \quad I_E = I_C + I_B$$

$$I_B R_s + 2R_E (\beta + 1) I_B + V_{BE} - V_{EE} = 0$$

$$I_B [R_s + 2R_E (\beta + 1)] = V_{EE} - V_{BE} \quad \text{--- (2)}$$

$$\frac{I_C}{\beta} [R_s + 2R_E (\beta + 1)] = V_{EE} - V_{BE}$$

$$I_{CQ} = I_C = \frac{V_{EE} - V_{BE}}{\frac{R_s}{\beta} + 2R_E (\beta + 1)}$$

let $\frac{\beta + 1}{\beta} \approx 1$

$$I_C = \frac{V_{EE} - V_{BE}}{\frac{R_s}{\beta} + 2R_E}$$

If source is ideal i.e. its internal resistance is neglected

$$I_{CQ} = \frac{V_{EE} - V_{BE}}{2R_E}$$

$$\rightarrow I_B R_s + V_{BE} + V_E = 0$$

$$\therefore I_B R_s < V_{BE}$$

$$V_{BE} + V_E = 0$$

$$V_E = -V_{BE}$$

$$V_C = V_{CC} - I_C R_C \quad V_{CE} = V_C - V_E$$

$$V_{CEQ} = V_{CE} = V_{CC} - I_C R_C - (-V_{BE})$$

$$V_{CEQ} = V_{CE} = V_{CC} - I_C R_C + V_{BE}$$

Q. The following specifications are given for the dual input balanced output differential amplifier, $R_C = 2.2 \text{ k}\Omega$, $V_{EE} = 10 \text{ V}$, $R_E = 4.7 \text{ k}\Omega$, $\beta_{dc} = 100$, $V_{CC} = 10 \text{ V}$, $R_s = 50 \Omega$, $V_{BE} = 0.715 \text{ V}$

Determine the operating points of 2 transistors

$$\rightarrow R_C = 2.2 \text{ k}\Omega, R_E = 4.7 \text{ k}\Omega, R_s = 50 \Omega, V_{CC} = 10 \text{ V}, V_{EE} = 10 \text{ V}, \beta_{dc} = 100, V_{BE} = 0.715 \text{ V}$$

$$V_{CEQ} = 10 - I_C \times 2.2 \text{ k}\Omega + 0.715 \text{ V}$$

$$I_C = 10 - .715$$



$$\frac{50}{100} + \frac{2 \times 4.7 \times 10^3}{100} + 2 \times 4.7 \times 10^3$$

$$I_C = .00097793 = .9779 \text{ mA}$$

$$V_{CQ} = 10 - .9779 \times 10^{-3} \times 2.2 \times 10^3 + .715$$

$$= 0.56362 \text{ V}$$

AC analysis of differential amplifier

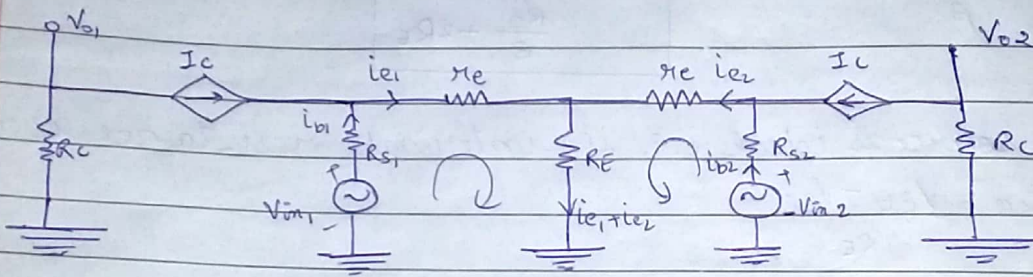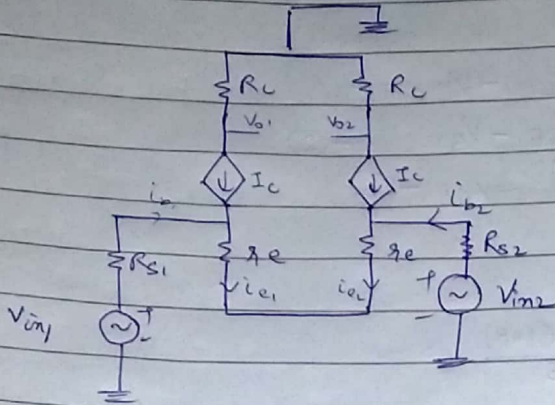

$$V_{in1} - i_{b1} R_{S1} - i_{e1} r_{e1} - R_E (i_{e1} + i_{e2}) = 0$$

$$V_{in2} - i_{b2} R_{S2} - i_{e2} r_{e2} - R_E (i_{e1} + i_{e2}) = 0$$

$$V_{in1} - \frac{i_{e1} R_{S1}}{\beta_{ac}} - i_{e1} r_{e1} - R_E (i_{e1} + i_{e2}) = 0 \quad \left\{ \begin{array}{l} i_{e1} \frac{R_{S1}}{\beta_{ac}} \ll 1 \end{array} \right.$$

assumption

$$i_c = \beta_{ac} i_b$$

$$i_e = i_c + i_b$$

$$i_e \approx i_c$$

$$i_e = \beta_{ac} i_b$$

$$i_b = \frac{i_e}{\beta_{ac}}$$

$$V_{in2} - \frac{i_{e2} R_{S2}}{\beta_{ac}} + i_{e2} r_{e2} - R_E (i_{e1} + i_{e2}) = 0 \quad \left\{ \begin{array}{l} \therefore \frac{R_{S2} i_{e2}}{\beta_{ac}} \ll 1 \end{array} \right.$$

$$V_{in1} - i_{e1} R_E - R_E (i_{e1} + i_{e2}) = 0$$

$$V_{in2} - i_{e2} R_E - R_E (i_{e1} + i_{e2}) = 0$$

$$V_{in1} - i_{e1} (\pi_e + R_E) - R_E i_{e2} = 0 \Rightarrow V_{in1} = i_{e1} (\pi_e + R_E) + R_E i_{e2} \quad] \times (\pi_e + R_E) \text{ --- (I)}$$

$$V_{in2} - i_{e2} (\pi_e + R_E) - R_E i_{e1} = 0 \Rightarrow V_{in2} = i_{e2} (\pi_e + R_E) + R_E i_{e1} \quad] \times R_E \text{ --- (II)}$$

Solving (I) & (II)

$$V_{in1} (\pi_e + R_E) = i_{e1} (\pi_e + R_E)^2 + R_E i_{e2} (\pi_e + R_E)$$

$$V_{in2} R_E = i_{e1} R_E^2 + i_{e2} R_E (\pi_e + R_E)$$

$$V_{in1} (\pi_e + R_E) - V_{in2} R_E = i_{e1} [(\pi_e + R_E)^2 - R_E^2]$$

$$i_{e1} = \frac{V_{in1}(g_e + R_E) - V_{in2} R_E}{(g_e + R_E)^2 - R_E^2}$$

$$i_{e2} = \frac{V_{in2}(g_e + R_E) - R_E V_{in1}}{(R_E + g_e)^2 - R_E^2}$$

$$V_o = V_{c1} - I_{c1} R_c \Rightarrow V_o = -I_{c1} R_c$$

$$V_{o1} = -i_{c1} R_c$$

$$V_{o2} = -i_{c2} R_c$$

$$V_o = V_{o2} - V_{o1} \quad \frac{V_o}{V_{o1} + V_{o2}}$$

$$V_o = -i_{c2} R_c - (-i_{c1} R_c)$$

$$= -i_{c2} R_c + i_{c1} R_c$$

$$= i_{c1} R_c - i_{c2} R_c$$

$$V_o = R_c (i_{c1} - i_{c2})$$

$$\therefore i_c = i_e$$

$$\therefore i_{c1} = i_{e1}$$

$$\text{and } i_{c2} = i_{e2}$$

$$V_o = R_c (i_{e1} - i_{e2})$$

$$V_o = R_c \left\{ \frac{V_{in1}(g_e + R_E) - V_{in2} R_E}{(g_e + R_E)^2 - R_E^2} - \frac{V_{in2}(g_e + R_E) - R_E V_{in1}}{(g_e + R_E)^2 - R_E^2} \right\}$$

$$= R_c \left[\frac{V_{in1}(g_e + R_E) - V_{in2} R_E - V_{in2}(g_e + R_E) + R_E V_{in1}}{(g_e + R_E)^2 - R_E^2} \right]$$

$$= R_c \left\{ \frac{V_{in1}(g_e + 2R_E) - V_{in2}(g_e + 2R_E)}{(g_e + R_E)^2 - R_E^2} \right\}$$

$$= R_c \frac{(g_e + 2R_E)(V_{in1} - V_{in2})}{(g_e + R_E)^2 - R_E^2} = R_c \frac{(g_e + 2R_E)(V_{in1} - V_{in2})}{g_e^2 + R_E^2 + 2g_e R_E - R_E^2}$$

$$= R_c \frac{(g_e + 2R_E)(V_{in1} - V_{in2})}{g_e(g_e + 2R_E)}$$

$$= R_c \frac{(V_{in1} - V_{in2})}{g_e}$$

$$V_o = R_c \frac{(V_{in1} - V_{in2})}{g_e}$$

$$V_d = V_{in1} - V_{in2}$$

$$V_o = \frac{R_c}{g_e} V_d$$

$$A_d = \frac{V_o}{V_d} = \frac{R_c}{g_e}$$

$r_e = \frac{26mV}{I_E}$ $I_E =$ DC emitter current it will be obtained from DC analysis $I_{CQ} = \frac{V_{CC} - V_{CE}}{2R_E}$ and $I_E \approx I_{CQ}$

Input impedance $R_{i1} |_{V_{in2}=0}$, $R_{i2} |_{V_{in1}=0}$

$R_{i1} = \frac{V_{in1}}{i_{b1}}$ and $i_{b1} = \frac{i_{e1}}{\beta_{ac}}$
 $V_{in2} = 0$

$\therefore R_{i1} = \frac{V_{in1}}{i_{e1}/\beta_{ac}}$ $V_{in2} = 0$

$R_{i1} = \frac{V_{in1} \beta_{ac}}{i_{e1}}$ $V_{in2} = 0$

$R_{i1} = \frac{V_{in1} \beta_{ac}}{V_{in1} \times \beta_{ac} \times r_e (\beta_{ac} + 2R_E)}$
 $\frac{V_{in1} (\beta_{ac} + R_E) - 0}{(\beta_{ac} + R_E)^2 - R_E^2}$

$= \frac{\beta_{ac} r_e (\beta_{ac} + 2R_E)}{\beta_{ac} + R_E}$


$\therefore r_e \ll R_E$ $\therefore \beta_{ac} \ll R_E$

$R_{i1} = \frac{\beta_{ac} r_e (2R_E)}{R_E}$


\therefore input impedance, $R_{i1} = 2 \beta_{ac} r_e$

Different configuration of differential amplifier

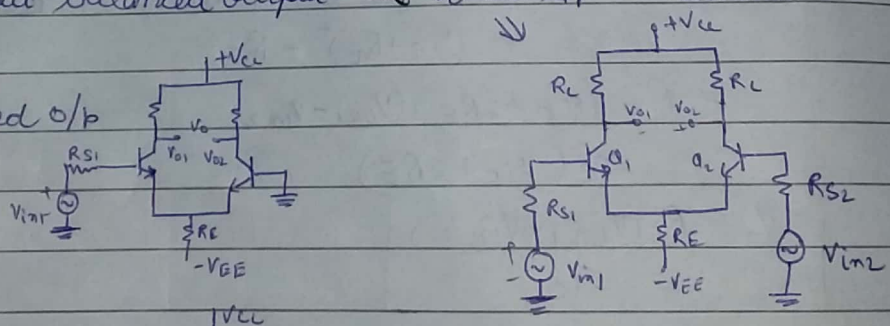
i) Differential input balanced output OR dual i/p balanced o/p




ii) single i/p balanced o/p

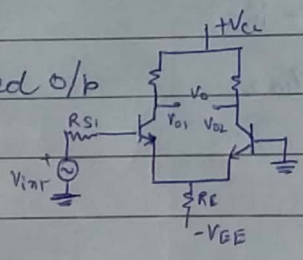


iii) single i/p unbalanced o/p

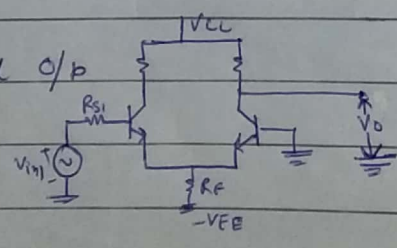

iv) Dual i/p unbalanced o/p

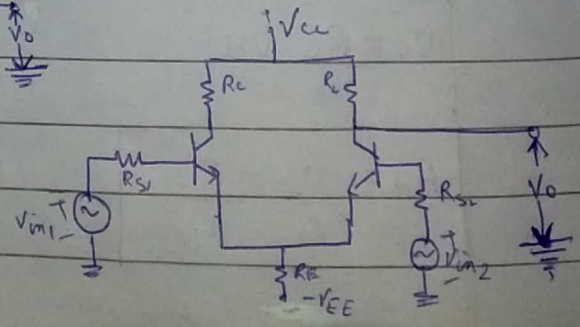

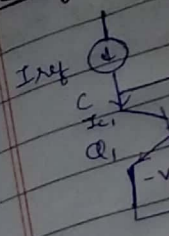Current $I_{in} \rightarrow$ CM $I_o = I_{in}$ Stages of




Require

- 1.) idll
- 2.) Idler


$I_{B1} =$
 $I_{C1} =$

3.) AE
a
em

Current mirror

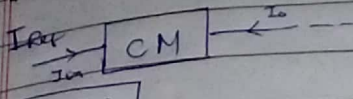

Stages of current mirror

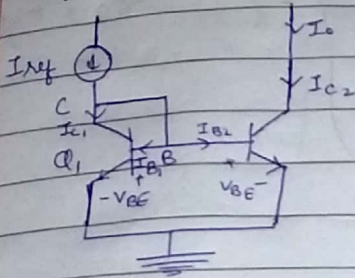

Required assumption for current mirror

- 1) All $Q \rightarrow$ active region
- 2) Identical (matched) transistors

$$I_{B1} = I_{B2} \quad V_{CE1} = V_{CE2} = V_{CE}$$

$$I_{C1} = I_{C2} \quad \beta_1 = \beta_2 = \beta$$

$$3) A_{E2} = A_{E1}$$

area of emitter base junction of transistor 1 is equal to area of emitter base junction of transistor 2.

$$I = I_{B1} + I_{B2} \quad \text{--- (1) (apply KCL at B)}$$

$$\text{as } I_{B1} = I_{B2} = I_B \quad \text{--- (2)}$$


$$I = 2 I_B \quad \text{--- (3)}$$

$$I_{ref} = I_C + I \quad \text{--- (4)}$$

$$I_{ref} = I_C + 2 I_B \quad \text{--- (5)}$$

$$I_0 = \beta I_B \quad \text{--- (6)}$$

$$I_0 = \beta I_B \quad \text{--- (7)}$$

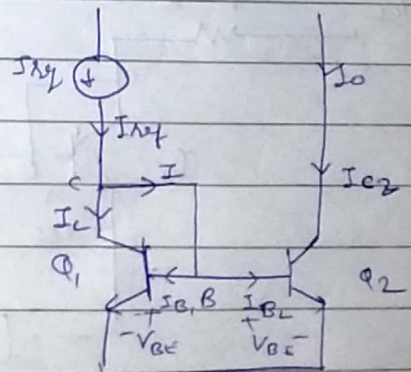

$$I_{ref} = \beta I_0 + 2 I_B$$

$$I_{ref} = (\beta + 2) I_B \quad \text{--- (8)}$$

divide (7) & (8)

if Q_2 is high $I_o > I_{ref}$
 if Q_2 is low i.e. $Q_2 < Q_1$, then $I_o < I_{ref}$

$$\frac{I_{ref}}{I_o} = \frac{(B+2) I_B}{B I_B}$$

$$\frac{I_{ref}}{I_o} = \frac{B+2}{B}$$

$$I_{ref} = I_o \left(\frac{B+2}{B} \right)$$

$$I_o = I_{ref} \left(\frac{B}{B+2} \right)$$

if B is low

if areas are equal

if no data given

if B is very high


$$I_o \approx I_{ref}$$

$B \rightarrow \infty$
 $I_B \rightarrow \frac{I_C}{B} \rightarrow I_C \rightarrow \infty$
 $\therefore I_o = I_{ref}$

If $A_{E2} = 2 A_{E1}$ (i.e. if areas are not equal)


$$\frac{I_o}{I_{ref}} = \frac{A_{E2}}{A_{E1}} \left(\frac{B}{B+2} \right)$$

$\Leftarrow B$ is high

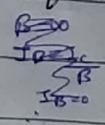

$$\frac{I_o}{I_{ref}} = \frac{A_{E2}}{A_{E1}} \left(\frac{B}{B+2} \right) \Leftarrow B \text{ is low}$$

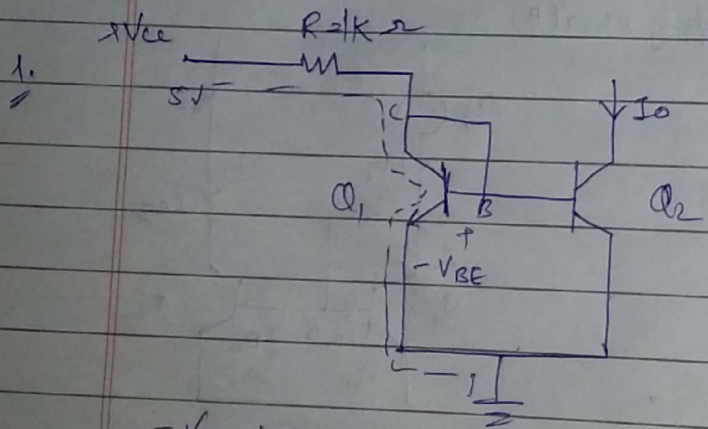If there is no current source then calculation of I_{ref}





$$-V_{cc} + I_{ref} R + V_{BE} = 0$$

$$I_{ref} R = V_{cc} - V_{BE}$$


$$I_{ref} = \frac{V_{cc} - V_{BE}}{R}$$

C & B are shorts so collector base junction is not considered

2. $I_o = 5 \text{ mA}$
 $R = ?$

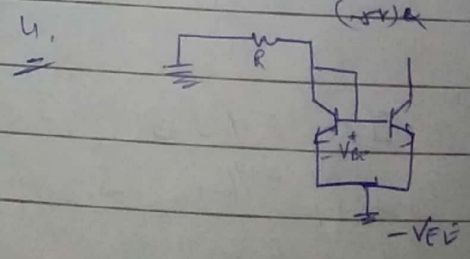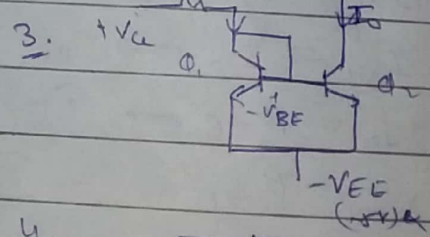

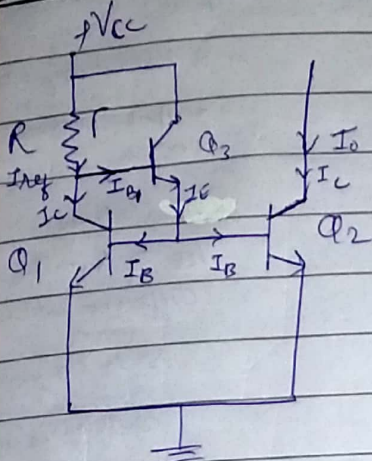Improved current mirror using base current compensation



~~for Q3~~ for Q3 $I_E = 2I_B$ — (1)

$$I_{B1} = \frac{I_E}{\beta + 1}$$

$$I_{B1} = \frac{2I_B}{\beta + 1}$$
 — (2)

$$I_{ref} = I_c + I_{B1}$$

$$= I_c + \frac{2I_B}{\beta + 1}$$

$$= \beta I_B + \frac{2}{\beta + 1} I_B$$

$$I_{ref} = I_B \left(\frac{\beta + 2}{\beta + 1} \right)$$
 — (3)

for Q2

$$I_o = \beta I_B$$
 — (4)

(4)/(3)

$$\frac{I_o}{I_{ref}} = \frac{\beta I_B}{I_B \left(\frac{\beta + 2}{\beta + 1} \right)}$$

$$= \frac{\beta}{\frac{\beta + 2}{\beta + 1}}$$

$$= \frac{\beta}{\frac{\beta^2 + \beta + 2}{\beta + 1}}$$

$$\frac{I_o}{I_{ref}} = \frac{\beta(\beta + 1)}{\beta^2 + \beta + 2}$$
 — (B)

Comparing (A) & (B)

$$I_o = I_{ref} \left(\frac{\beta}{\beta + 2} \right)$$

$$I_o = I_{ref} \frac{(\beta^2 + \beta)}{\beta^2 + \beta + 2}$$

for $\beta = 100$

$$I_o = I_{ref} \left(\frac{100}{102} \right)$$


$$I_o = I_{ref} \left(\frac{10000 + 100}{10000 + 100 + 2} \right)$$

$$I_o = I_{ref} \left(\frac{10100}{10102} \right)$$

$$I_o = I_{ref} (0.9803)$$

$$I_o = I_{ref} (0.9998)$$

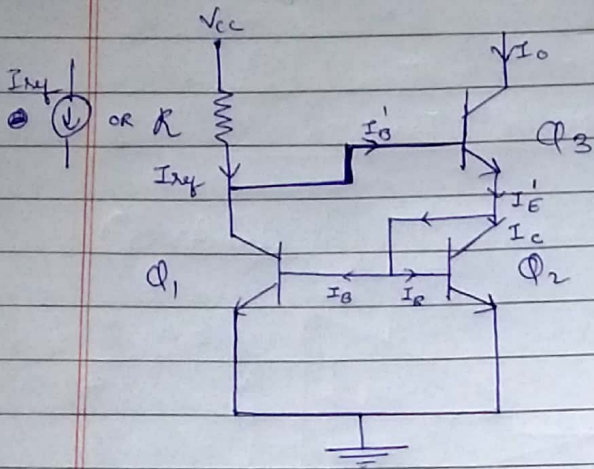Wilson current mirror (Wilson current source)



Adv.

- β dependency will decrease
- output resistance will increase

Limitations

V_{CE} of Q_1, Q_2 are different which is producing error
 So to compensate the error, an improved version is introduced

$$I_{E'} = 2I_B + I_C$$

$$I_{E'} = \frac{2I_C + I_C}{\beta}$$

$$I_{E'} = I_C \left(\frac{2}{\beta} + 1 \right) \quad \text{--- (1)}$$

$$I_B' = \frac{I_{E'}}{\beta + 1}$$

$$I_B' = I_C \left(\frac{1 + 2/\beta}{\beta + 1} \right) \quad \text{--- (2)}$$

$$I_{ref} = I_C + I_B'$$

$$I_{ref} = I_C + I_C \left(\frac{1 + 2/\beta}{\beta + 1} \right)$$

$$I_{ref} = I_C \left(1 + \frac{1 + 2/\beta}{\beta + 1} \right) \quad \text{--- (3)}$$

$$I_O = \beta I_B'$$


$$I_O = \beta \left[I_C \left(\frac{1 + 2/\beta}{\beta + 1} \right) \right] \quad \text{--- (4)}$$

(4)/(3)

$$\frac{I_O}{I_{ref}} = \frac{1}{1 + \frac{1}{\beta^2 + 2\beta}}$$

$I_0 = I_{ref}$
 $I_{ref} = \frac{V_{cc} - V_{BE}}{R}$
 $V_{BE} = \frac{I R}{\beta + 1}$

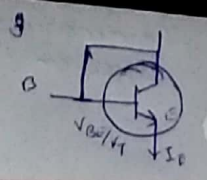
Limitation
 If I in μA , we have
 to use high resistance
 and high resistance
 takes large chip area
 as compared to another circuit




Diode connected transistor
 $I_E = I_{sc}$

Date: ___/___/___

Improved Wilson current mirror

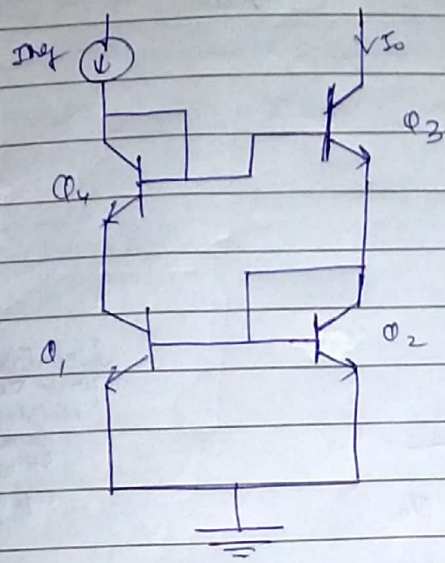

Widlar current source / current mirror

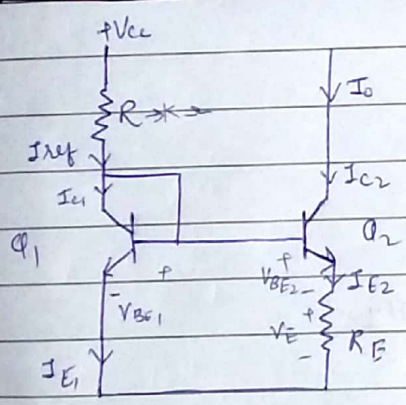

In Widlar, $I_o \neq I_{ref}$, I_o depends on R_E hence R is not
 in MS
 app. \rightarrow low value of current source in μA
 \propto DSA

$$I_{E1} = I_s e^{\frac{V_{BE1}}{V_T}} \quad - (1)$$

$$V_{BE2} = V_T \ln \left(\frac{I_o}{I_s} \right) \quad - (4)$$

$$I_{E2} = I_s e^{\frac{V_{BE2}}{V_T}} \quad - (2)$$

$$-V_{BE1} + V_{BE2} + V_E = 0$$

$$I_C \cong I_{E1} = I_{ref}$$

$$I_{C2} = I_{E2} = I_o$$

$$I_{E2} R_E = V_{BE1} - V_{BE2}$$

$$I_o R_E = V_{BE1} - V_{BE2}$$

$$I_o = \frac{V_{BE1} - V_{BE2}}{R_E} \quad - (5)$$

$$\frac{I_{ref}}{I_s} = e^{\frac{V_{BE1}}{V_T}}$$

$$\ln \left(\frac{I_{ref}}{I_s} \right) = \frac{V_{BE1}}{V_T}$$

$$V_{BE1} = V_T \ln \left(\frac{I_{ref}}{I_s} \right) \quad - (3)$$

freq. response
 it is the ability of device to response to a wide range of frequencies with some accuracy.

Common mode rejection ratio


$$CMRR = \left| \frac{A_{od}}{A_{cm}} \right|$$

Date: ___/___/___

$$I_o = \frac{1}{R_E} \left[V_T \ln \left(\frac{I_{ref}}{I_s} \right) - V_T \ln \left(\frac{I_o}{I_s} \right) \right]$$

$$I_o = \frac{V_T}{R_E} \left[\ln \left(\frac{I_{ref}}{I_o} \right) \right]$$

Op-Amp

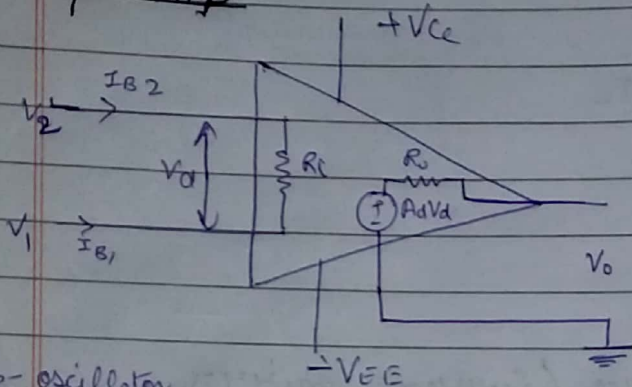

Isolator

first circuit isolated from the second circuit. It helps in case if first circuit get short circuit then in that case second circuit remain safe.

app- oscillator


1) Input impedance

	Ideal	Practical
1) R_i	∞	$\geq 10^5 \Omega$
2) A_{cl}	∞	$\geq 10^4$
3) $CMRR$	∞	$\geq 70dB$
4) Bandwidth	∞	approx 1MHz

$V_d = v_1 - v_2$
 $v_1 = v_2$
 $v_1 = \infty$
 $v_o = A_{cl} v_d = 0$
 $A_{cm} = \frac{A_{od}}{A_{cm}} = \infty$
 $CMRR = \frac{A_{od}}{A_{cm}} = \infty$

Current to voltage converter

(I-V converter)

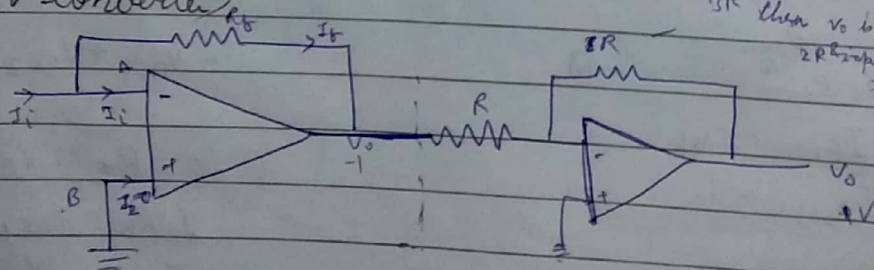


3R and input -1 then $v_o = 3V$
 2R input and -1 then $v_o = 2V$

$I_i = I_f + I$
 $I_i = I_f$
 $0 - V_o = I_f R_f$
 $V_o = -I_f R_f$

Inverter with unity gain

Voltage to current converter

i) VI converter with floating load

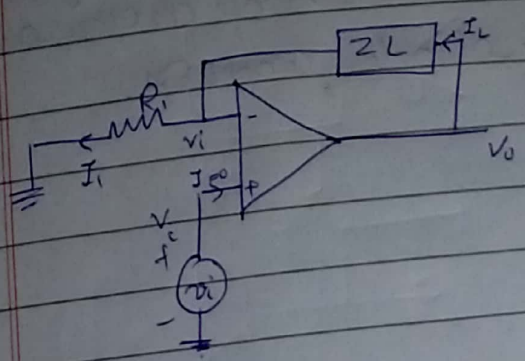


$$I_1 = I_L$$

$$I_1 = \frac{V_i - 0}{R}$$

$$I_1 = \frac{V_i}{R}$$

$$I_L = \frac{V_i}{R}$$

ii) VI converter with grounded load

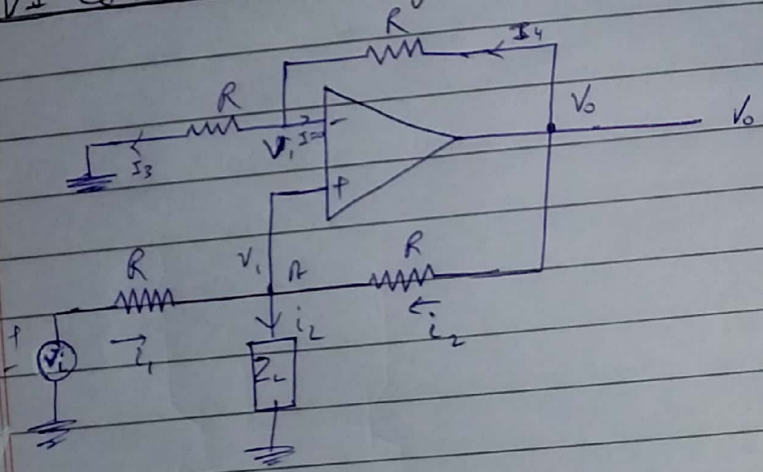

KCL at node A

$$i_1 = i_2 + i_L$$

$$i_1 = \frac{V_i - V_1}{R}$$

$$i_2 = \frac{V_0 - V_1}{R}$$

$$V_3 = V_4$$

$$\frac{V_i - 0}{R} = \frac{V_0 - V_1}{R}$$

$$V_i = V_0 - V_1$$

$$\boxed{V_0 = 2V_i}$$

$$i_L = \frac{V_i - V_1}{R} + \frac{V_0 - V_1}{R}$$

$$i_L = \frac{V_i + V_0 - 2V_1}{R}$$

Substituting

$$\boxed{i_L = \frac{V_i}{R}}$$

Adde, subtrac,
differentials, integration

Applications


V-I converters are used, in low amp. of voltage measurement, low amp current measurement devices and testing circuits for zener diodes and LEDs.

Applications


V-I converters are used in low amp. of voltage measurement, low amp current measurement devices and testing circuits for zener diodes and LEDs.

used as diff. amp.

Instrumentation Amplifier

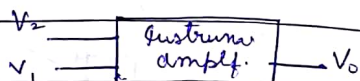

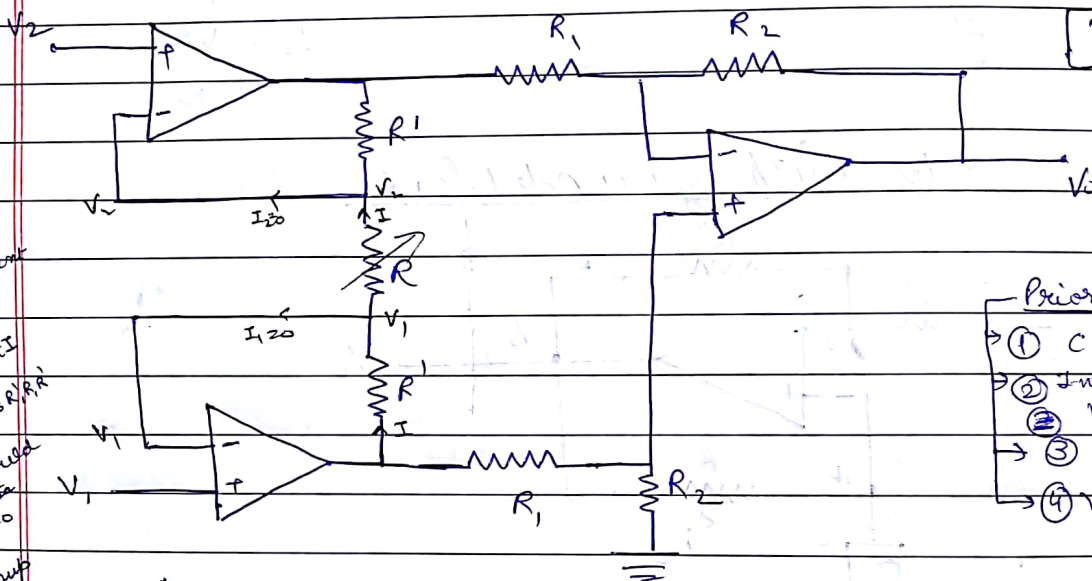
$V_o \propto (V_1 - V_2)$
 $V_o = A(V_1 - V_2)$



If $V_1 = V_2$ then I_{20} and no current will flow from R

Some current I will flow through all 5 R's and $V_2 \neq V_1$ current should get distributed but I_1 & $I_2 = 0$ keep input imp of Op-amp is very high

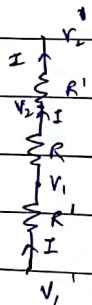- Priorities advantages
- ① CMRR = ∞
 - ② Input offset = 0
 - ③ Voltage
 - ③ $R_i = \infty$
 - ④ Voltage = 0



$V_1' = V_1 + IR'$

$I = \frac{V_1 - V_2}{R}$ (3)

$V_1 = V_1' - IR'$ (1)


$V_2 = V_2' + IR'$ (2)

from ①, ② & ③

$V_1 = V_1' - \frac{(V_1 - V_2)R'}{R}$ (4)

$V_2 = V_2' + \frac{(V_1 - V_2)R'}{R}$ (5)

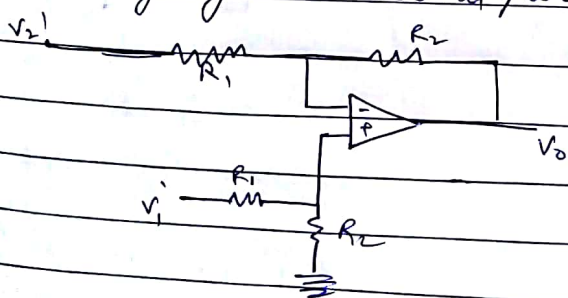
Now analyzing the second part of the circuit,



By superposition

Case 1

$V_2' = 0$

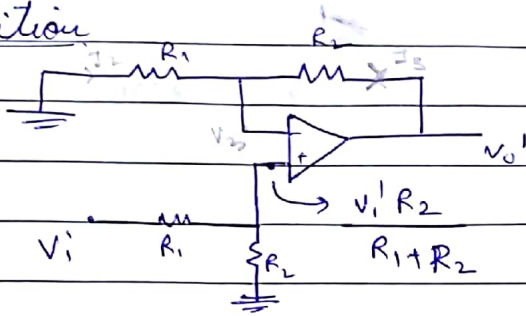

$I_2 = I_3$
 $\frac{0 - V_2}{R_1} = \frac{V_3 - V_0}{R_2}$

$0 - \frac{V_1' R_2}{R_1 + R_2} = \frac{V_1' R_2}{R_1 + R_2} - V_0$

$V_0' = \left(1 + \frac{R_2}{R_1}\right) \frac{V_1' R_2}{R_1 + R_2}$
 $V_0' = \left(\frac{R_1 + R_2}{R_1}\right) \frac{V_1' R_2}{R_1 + R_2}$


output of inverting amplifier

$V_0 = \left(1 + \frac{R_2}{R_1}\right) \frac{V_1' R_2}{R_1 + R_2}$

$V_0' = V_1' \frac{R_2}{R_1}$

$V_0 = \left(1 + \frac{R_2}{R_1}\right) V_1'$

Case 2

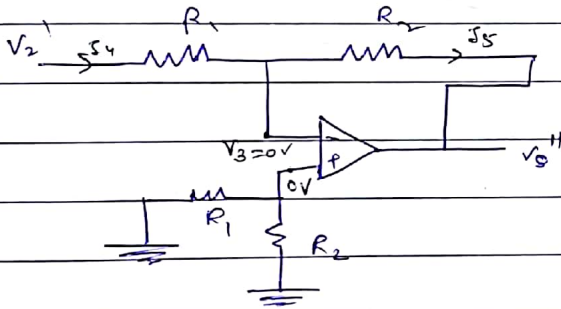

$V_1' = 0$

$I_4 = I_5$

$\frac{V_2' - 0}{R_1} = 0 - \frac{V_0''}{R_2}$

$V_2' = -\frac{V_0''}{R_2} R_1$

$V_0'' = -\frac{R_2}{R_1} V_2'$

$V_0'' = -\frac{R_2}{R_1} V_2'$


$V_0 = V_0' + V_0''$

$V_0 = V_1' \frac{R_2}{R_1} - V_2' \frac{R_2}{R_1} \Rightarrow V_0 = \frac{R_2}{R_1} (V_1' - V_2') \quad \text{--- (6)}$

CONCEPTS: COMBIN
 (LECTOR)

carry several digital
 in short intervals at
 the transmitting end
 received signal on
 change in one
 must be provided
 will select one

Date ___ / ___ / ___

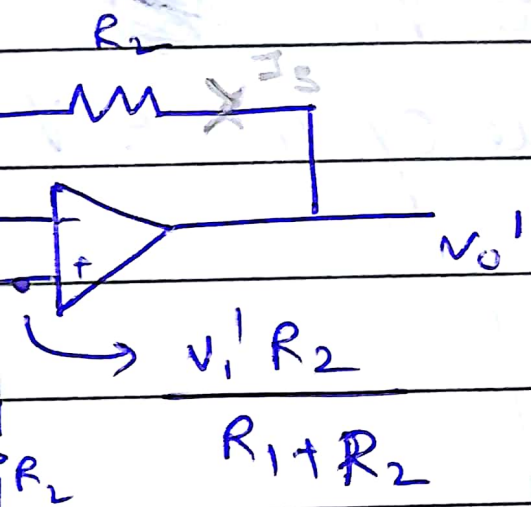

$$I_2 = I_3$$

$$\left\{ \frac{0 - V_2}{R_1} = \frac{V_3 - V_0}{R_2} \right\}$$

$$V_0' = \left(1 + \frac{R_2}{R_1} \right) \frac{V_1' R_2}{R_1 + R_2}$$

$$V_0' = \left(\frac{R_1 + R_2}{R_1} \right) \frac{V_1' R_2}{R_1 + R_2}$$

$$V_0' = V_1' \frac{R_2}{R_1}$$

dependency
of R_1

की जगह आ रहा है और R एक जगह इस लिए R variable होगा so to increase gain $R \rightarrow \downarrow$
4 \downarrow gain $R \rightarrow \uparrow$

Page No.

Date / /

~~Put the value of R & V_1 & V_2~~

Put the value of V_1 & V_2 from (4) & (5) in (6)

$$R_1 = R_2$$

this is
not
correct
eq
because this

$$V_0 = \frac{R'}{R} (V_1 - V_2)$$

the noise level means if a step signal is transition so that it will occur
 dependency of R_1 तो अगर आकरा है और R रुक जाए इसके R variable होगा so to increase \uparrow gain Δ
 decrease \downarrow gain Δ

Page No.

Date / /


Put the value of V_1' & V_2' from (4) & (5) in (6)
 $R_1 = R_2$

this is not correct eq solution


$$V_0 = \frac{R_1}{R_2} (V_1 - V_2)$$

II Module

Active filter

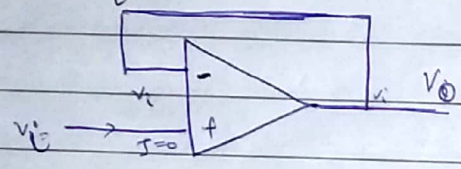

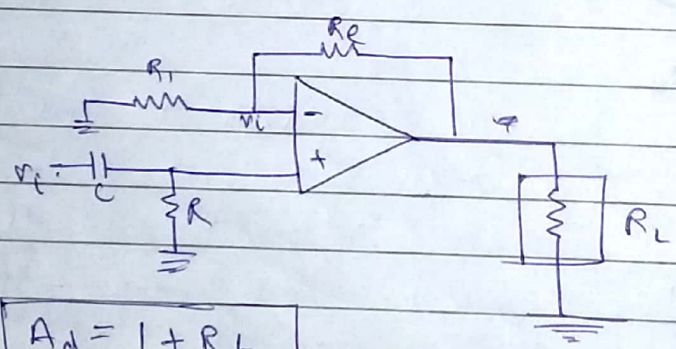Buffer, voltage ~~regulator~~ follower, unity gain amp, ~~etc~~
 adv as buffer is isolator.



$$A_d = 1 + \frac{R_2}{R_1}$$





\uparrow ve feedback \uparrow gain \downarrow stability
 \downarrow ve \downarrow gain \uparrow stability

Ideal filter \rightarrow

$$A = \frac{V_o}{V_{in}} = 1 \Rightarrow \text{Pass band}$$



$$A = 0 \Rightarrow \text{Stop band}$$

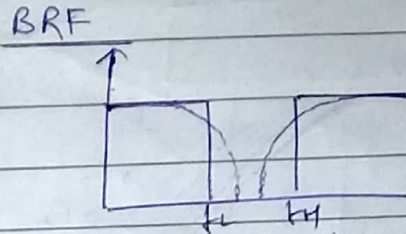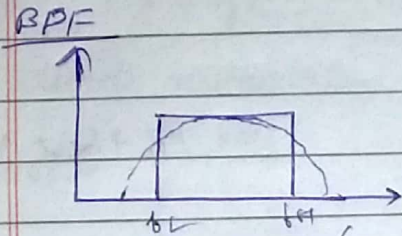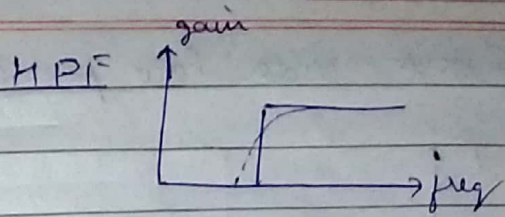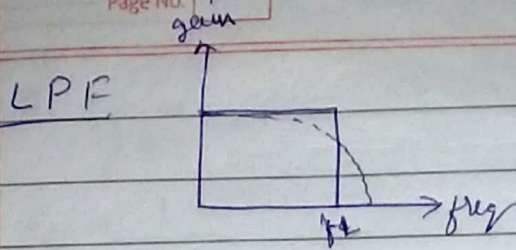- LPF
- HPF
- BPF \rightarrow Notch filter
- BRF (BSF)



Special case of BPF or BRF

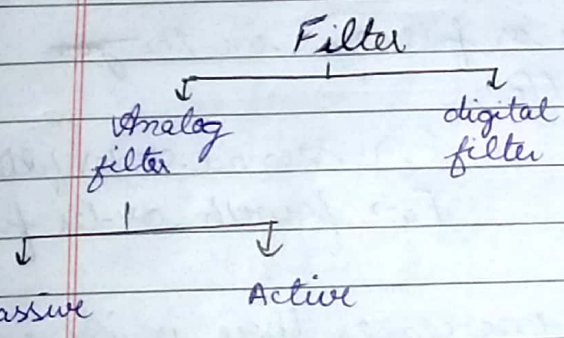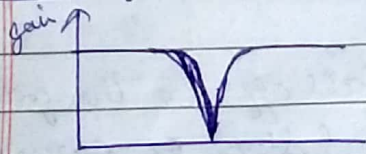
Notch filter (used to pass/reject a specific freq)



Passive → provide attenuation (drawback)
 can be compensated by active filter
 ○ loading effect

active → no attenuation
 ○ no loading effect

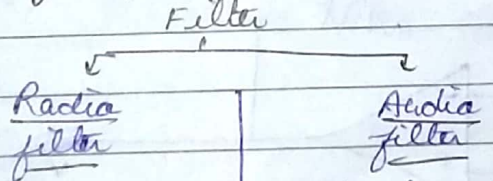
Based on range freq filter can be classified as



All pass filter
 ↓
 phase correction of received signal

Radio filter
 ○ filters used for high freq
 ○ L-C is used to determine cut off freq

Audio filter
 20Hz to 20KHz (used for low freq)
 ○ R-C is used or R-L but we prefer RC because of the size of L is large (can't we have to make inductor, we have to do the mathematics to design inductor) (also size of L is large at low freq)

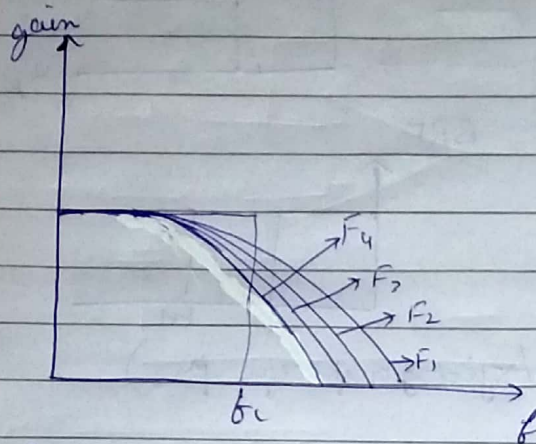First order low pass filter

F₄ + best response

Decrement in the gain is called fall off in the gain. F₄ has more rate of gain of change (slope of curve defines rate of change).

Rate of change of gain known as fall off in the gain defines order of the filter.


F₁ → first order filter

F₂ → second order filter

F₃ → third order filter

F₄ → fourth order filter

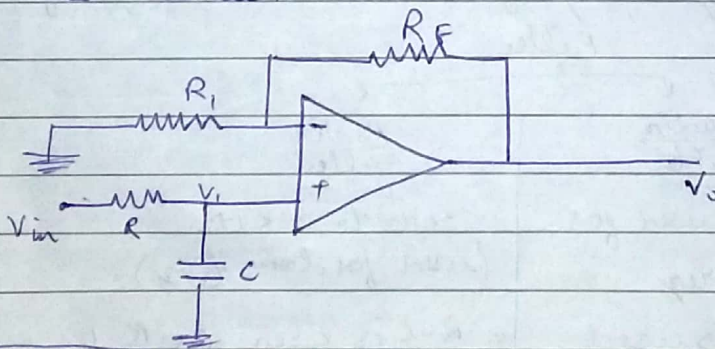As rate of change of gain increases there is increase in order, and as order increases, slope will reach towards ideal.



$$A_F = 1 + \frac{R_F}{R_i}$$

slope defines that it is first order

$$V_i = \frac{V_{in} \times X_C}{R + X_C} \quad \text{--- (1)}$$

$$X_C = \frac{1}{j\omega C}$$

$$X_C = \frac{1}{j 2\pi f C}$$

divide numerator of ① by X_C

$$V_i = \frac{V_i \times X_C}{\frac{R}{X_C} + \frac{X_C}{X_C}} = \frac{V_i}{\frac{R}{X_C} + 1}$$

$$V_i = \frac{V_i}{1 + j 2\pi f R C} \quad \text{②}$$

gain of amplifier

$$A_F = \frac{1 + R_F}{R_1}$$

$$V_o = A_F V_i = \frac{A_F V_i}{1 + j 2\pi f R C}$$

$$\frac{V_o}{V_i} = \frac{A_F}{1 + j 2\pi f R C} \quad \text{③}$$

$$\frac{V_o}{V_i} = \frac{A_F}{1 + j \frac{f}{f_c}} \quad \text{④}$$

By comparing

$$f_c = \frac{1}{2\pi R C} \quad \text{Cut off freq}$$

gain of filter

$$\left| \frac{V_o}{V_i} \right| = \frac{A_F}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

for $f \ll f_c$


$$\left| \frac{V_o}{V_i} \right| = A_F$$

for $f = f_c$

$$\left| \frac{V_o}{V_i} \right| = \frac{A}{\sqrt{2}} = 0.707 \times A$$

for $f \gg f_c$

$$\left| \frac{V_o}{V_i} \right| \ll A_F$$

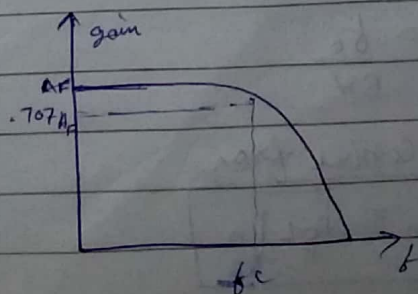


Bull-worm filter

Page No.

Band pass filter
 Date:
 Page No.
 Sing

2nd order low pass active filter

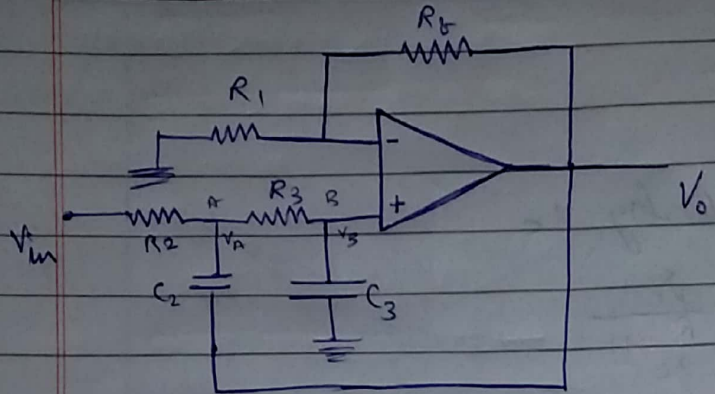


$$f_c = \frac{1}{2 \times \sqrt{R_2 C_2 R_3 C_3}}$$

$$R_2 = R_3 = R$$

$$C_2 = C_3 = C$$
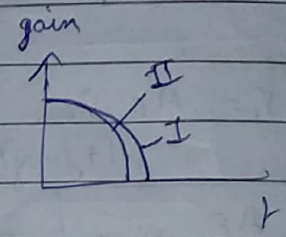
$$f_c = \frac{1}{2 \times RC} \quad \text{--- (1)}$$



$$\left| \frac{V_o}{V_i} \right| = \frac{A_f}{\sqrt{1 + \left(\frac{f}{f_c} \right)^2}} \quad \text{--- (2)}$$


$$A_f = 1.502$$

$$Q = 1.414$$

$$A_f = 3 - Q$$

$$A_f = 1.502$$

1 order high pass active filter

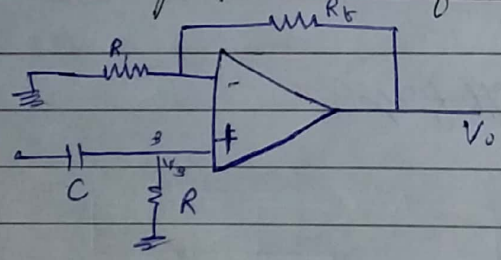

Band pass filter


1. Wide band pass filter ($f_L \rightarrow f_H$) $Q < 10$
2. Narrow band pass filter $Q > 10$


$$Q = \frac{f_0}{BW}$$

$$BW = f_H - f_L$$

$f_0 =$ Central freq

$$f_0 = \sqrt{f_L f_H}$$

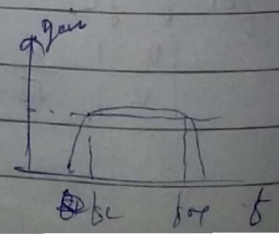

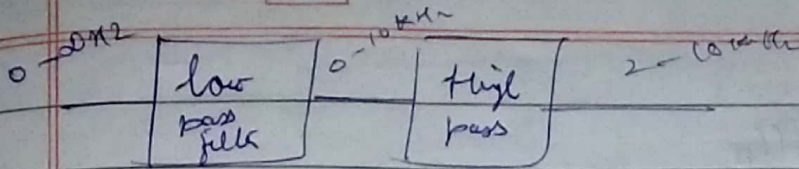

$f_H = 10\text{KHz}$

$f_L = 2\text{KHz}$

$$f_H = \frac{1}{2\pi R_2 C_2}$$


$$f_L = \frac{1}{2\pi R_3 C_3}$$

~~$A_T = A$~~

$$\left| \frac{V_o}{V_i} \right| = \frac{A_T \times \frac{f}{f_c}}{\sqrt{\left(1 + \left(\frac{f}{f_H}\right)^2\right)^2 \times \left(1 + \left(\frac{f}{f_L}\right)^2\right)^2}}$$

$$A_T = A_{F1} \times A_{F2}$$

Narrow band pass filter

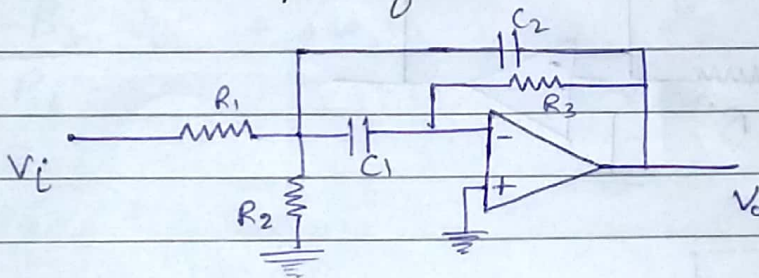

$$C_1 = C_2 = C$$

$$R_1 = \frac{\phi}{2\pi f_0 C A_F}$$

Quality factor gives information about the losses in the device if there are losses the quality is low and if losses are less the quality factor is high

Design a band pass filter so that $f_0 = 1\text{KHz}$, $A_F = 10$, $\phi = 3$

$$R_1 = \frac{\phi}{2\pi f_0 C A_F}$$

$C \leq 10\text{uF}$
 0.01uF

$$R_2 = \frac{\phi}{2\pi f_0 C (2\phi^2 - A_F)}$$

$$A_F = -\frac{R_3}{2R_1}$$

A_F for $f = f_0$

$$R_3 = \frac{\phi}{\pi f_0 C}$$

is that

Band pass

$f_H > f_L$

Date ___/___/___


Page No.

Band stop filter


- 1. Wide band stop filter
- 2. Narrow band stop filter

(Notch filter)

Wide band stop filter

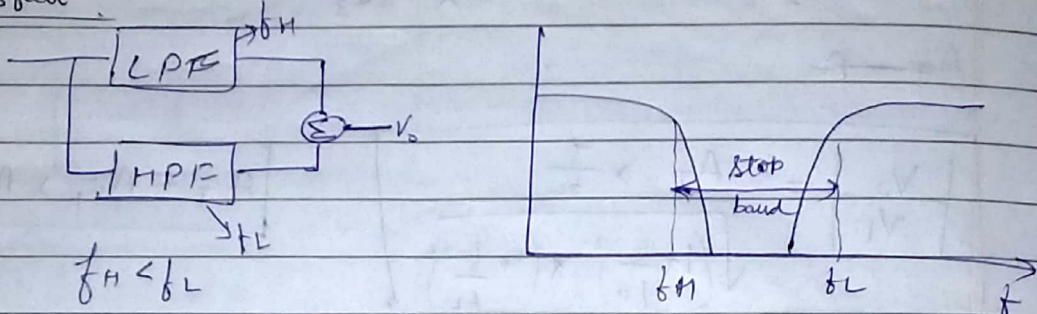

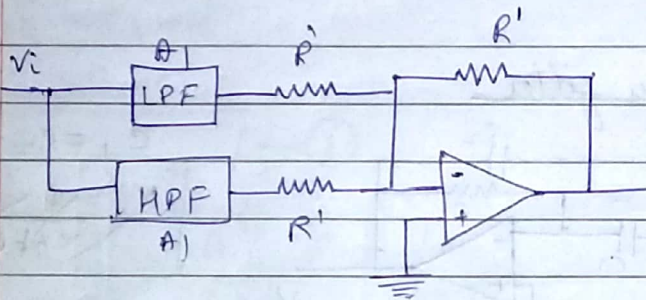
gain of LPE & HPE should be same otherwise the circuit will get unbalanced with each other



$$A_v = 1 + \frac{R_f}{R_i}$$

Narrow band stop filter (Notch filter)

Passive network

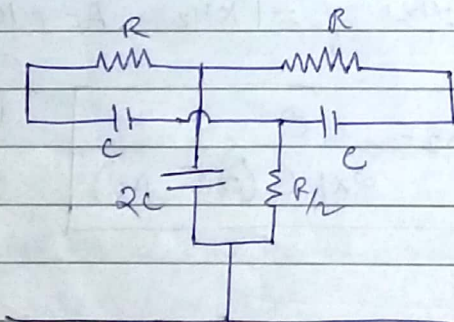



This filter has a low quality factor so we use op-amp to improve quality factor

Twin T network


$$f_n = \frac{1}{\sqrt{2}RC}$$

$f_n \rightarrow$ notch freq

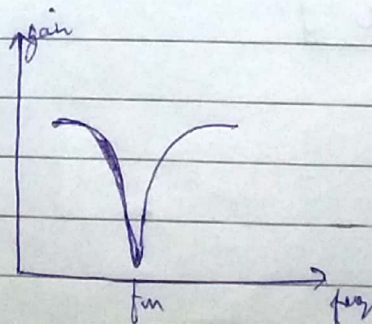


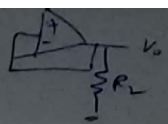

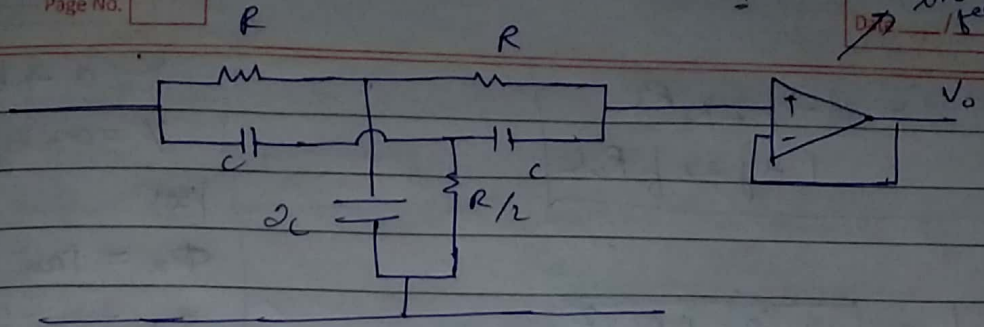this output also isolate load (it appears) from the circuit
 in unity feedback mode



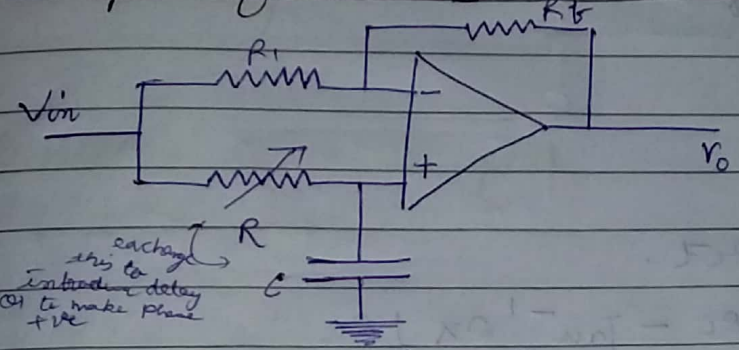All pass filter / Phase corrector / delay equalizer



exchange this to introduce delay to make phase +ve

By Super position theorem

$$V_o = \frac{-R_f}{R_1} V_{in} + \left(1 + \frac{R_f}{R_1}\right) \frac{V_{in} \times X_c}{R + X_c}$$

assume $R_f = R_1$

$$V_o = -V_{in} + \frac{2 V_{in} X_c}{R + X_c}$$

$$= -V_{in} + \frac{2 V_{in} X_c}{\frac{R + X_c}{X_c}}$$

$$V_o = -V_{in} + \frac{2 V_{in}}{\frac{R}{X_c} + 1}$$

$$V_o = -V_{in} + \frac{2 V_{in}}{R_f 2\pi f C + 1}$$

$$V_o = V_{in} \left(-1 + \frac{2}{1 + j 2\pi f RC} \right)$$

$$V_o = V_{in} \left(\frac{-1 - 2j 2\pi f RC + 2}{1 + j 2\pi f RC} \right)$$

$$V_o = V_{in} \left(\frac{1 - j 2\pi f RC}{1 + j 2\pi f RC} \right)$$

less phase shift factor

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1 - j2\pi f RC}{1 + j2\pi f RC}$$

$$X = a + bj$$

$$Y = a - bj$$

$$\phi_x = \tan^{-1} b/a$$

$$\phi_y = \tan^{-1} -b/a$$

$$= -\tan^{-1} b/a$$


$$\left| \frac{V_o}{V_{in}} \right| = \frac{\sqrt{1 + (2\pi f RC)^2}}{\sqrt{1 + (2\pi f RC)^2}}$$

$$\left| \frac{V_o}{V_{in}} \right| = 1$$


$$\phi = -\tan^{-1} 2\pi f RC$$


$$\phi = -\tan^{-1} 2\pi f RC - \tan^{-1} 2\pi f RC$$

$$\phi = -2 \tan^{-1} 2\pi f RC$$

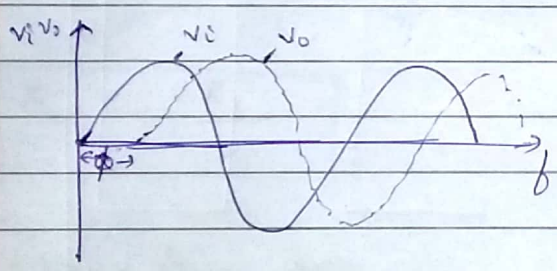


State variable filter

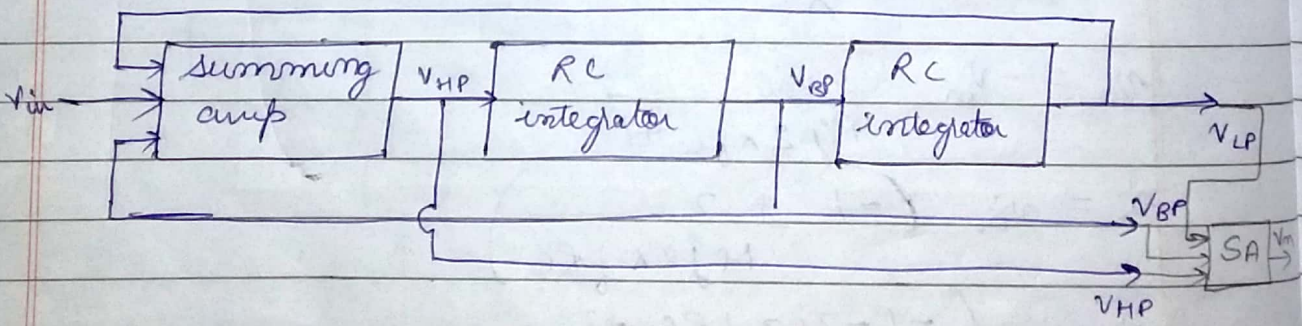

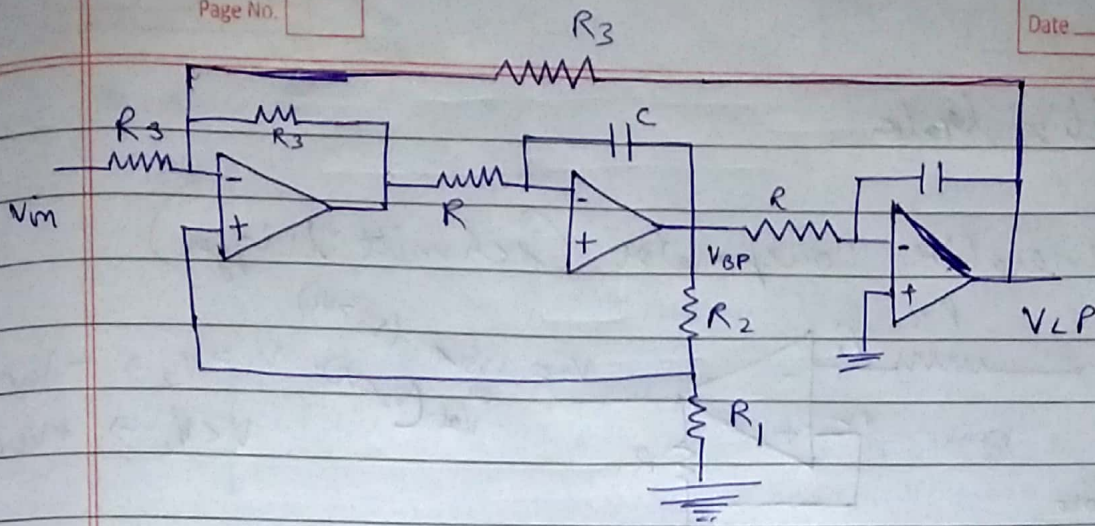

Switched capacitor filter

$$R = \frac{\rho L}{A}$$

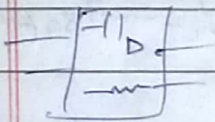

$$f = \frac{1}{\rho \pi R C} = 15.9 \text{ kHz}$$

$$R = 1 \text{ k}\Omega \quad C = 0.01 \mu\text{F}$$

$$Q_1 = CV_1$$

$$Q_2 = CV_2$$

$$Q = CV_1 - CV_2$$



$$Q = C(V_1 - V_2)$$

$$i = \frac{C(V_1 - V_2)}{t_{pk}}$$

$$t_{pk}$$

$$f_{ck} = \frac{1}{t_{ck}}$$

$$R = \frac{1}{C f_{ck}}$$

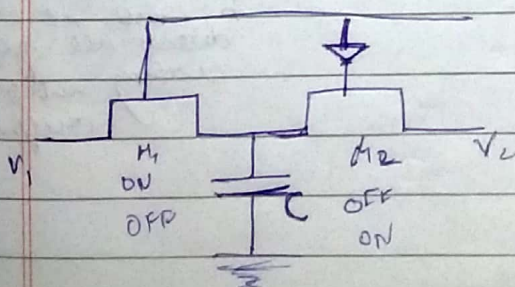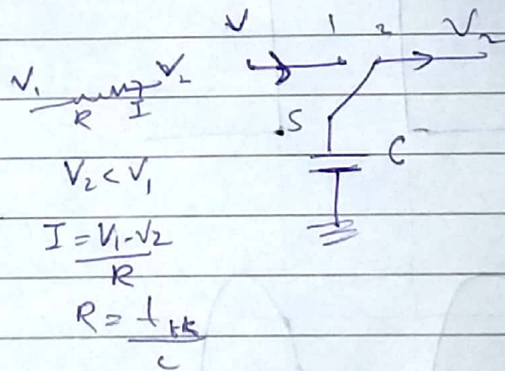


Multivibrator

1.) Regenerative Comparator (Schmitt trigger)

also known as




Sine to Square Wave Converter

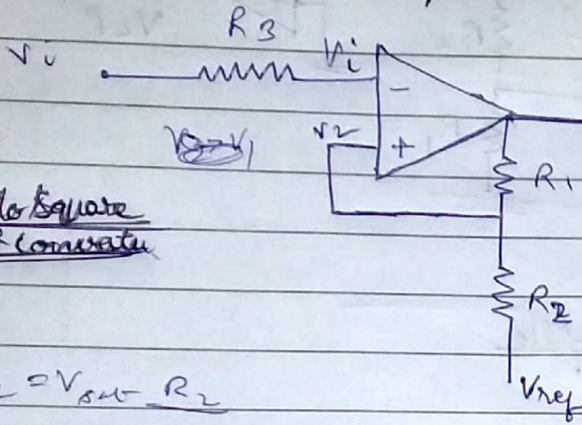

$V_0 = +V_{sat}$ ($V_2 > V_1$)
 $-V_{sat}$ ($V_2 < V_1$)
 $V_1 > V_2 \rightarrow -V_{sat}$
 $V_1 < V_2 \rightarrow +V_{sat}$

$V_2 = V_{sat} \cdot R_2$
 $V_2 = \beta(V_{sat})$ $R_1 + R_2$ $V_0 = +\beta V_{sat}$
 $V_2 = \beta V_{sat}$ $V_i = +\beta V_{sat}$

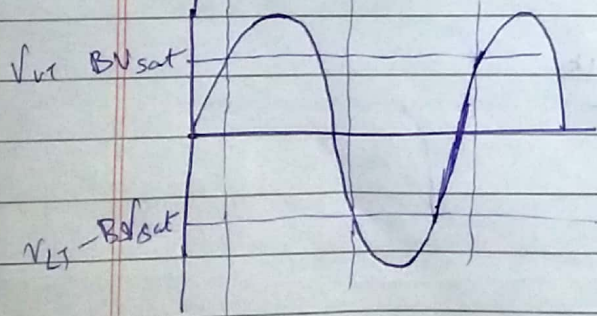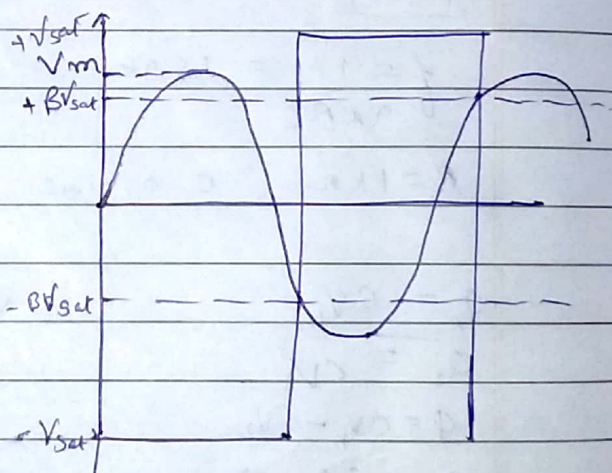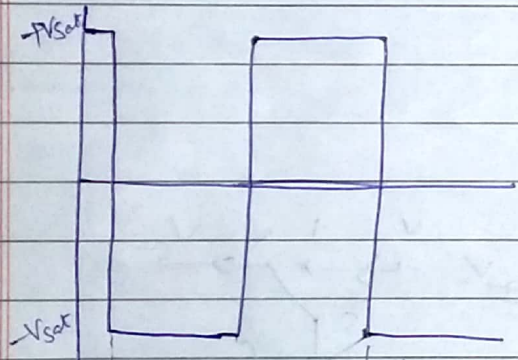By changing V_{UT} & V_{LT} duty cycle can be changed
 (upper threshold voltage) $V_{UT} = +\beta V_{sat}$
 $V_{LT} = -\beta V_{sat}$ (lower threshold voltage)
 $V_0 = -V_{sat}$
 $V_i = -\beta V_{sat}$




* V_m should be greater than V_{UT} otherwise it will not be trigger

point when the magnitude of the wave is same as known as switching points


$\beta < 1$
 $V_0 = +V_{sat}$
 $V_2 = \beta(+V_{sat})$
 $V_0 = -V_{sat}$
 $V_2 = \beta(-V_{sat})$

* It will not trigger on noisy signal because it will detect all zero crossing and give the output


output wave \rightarrow hysteresis

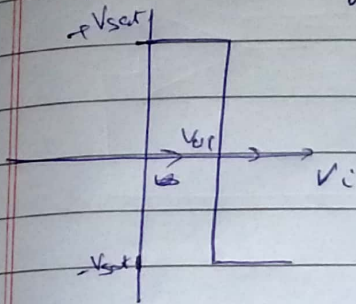

increase in input
when combined

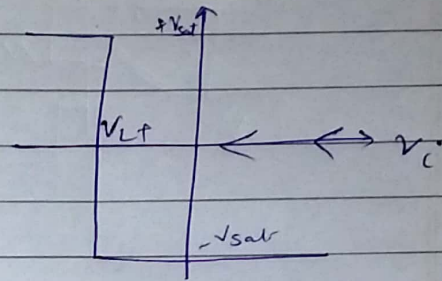

decrease in input

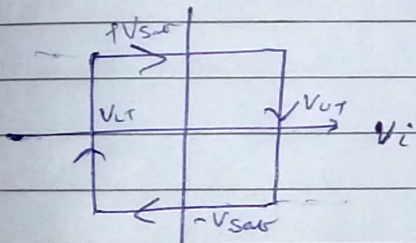

8-2 ACTIVE FILTERS

An electric filter is often a *frequency-selective* circuit that passes a specified band of frequencies and blocks or attenuates signals of frequencies outside this band. Filters may be classified in a number of ways:

1. Analog or digital
2. Passive or active
3. Audio (AF) or radio frequency (RF)
(LF)

transistor, R, L, C, OPAMP
R, L, C
High Freq

Analog filters are designed to process analog signals, while digital filters process analog signals using digital techniques. Depending on the type of elements used in their construction, filters may be classified as passive or active. Elements used in passive filters are resistors, capacitors, and inductors. Active filters, on the other hand, employ transistors or op-amps in addition to the resistors and capacitors. The type of element used dictates the operating frequency range of the filter. For example, RC filters are commonly used for audio or low-frequency operation, whereas LC or crystal filters are employed at RF or high frequencies. Especially because of their high Q value (figure of merit), the crystals provide more stable operation at higher frequencies.

First, this chapter presents the analysis and design of analog active-RC (audio-frequency) filters using op-amps. In the audio frequencies, inductors are often not used because they are very large, costly, and may dissipate more power. Inductors also emit magnetic fields.

An active filter offers the following advantages over a passive filter:

1. Gain and frequency adjustment flexibility. Since the op-amp is capable of providing a gain, the input signal is not attenuated as it is in a passive filter. In addition, the active filter is easier to tune or adjust.
2. No loading problem. Because of the high input resistance and low output resistance of the op-amp, the active filter does not cause loading of the source or load.
3. Cost. Typically, active filters are more economical than passive filters. This is because of the variety of cheaper op-amps and the absence of inductors.

Although active filters are most extensively used in the field of communications and signal processing, they are employed in one form or another in almost all sophisticated electronic systems. Radio, television, telephone, radar, space satellites, and biomedical equipment are but a few systems that employ active filters.

The most commonly used filters are these:

1. Low-pass filter
2. High-pass filter
3. Band-pass filter
4. Band-reject filter
5. All-pass filter

Each of these filters uses an op-amp as the active element and resistors and capacitors as the passive elements. Although the 741 type op-amp works satisfactorily in these filter circuits, high-speed op-amps such as the LM318 or ICL8017 improve the filter's performance through their increased slew rates and higher unity gain-bandwidths.

Figure 8-1 shows the frequency response characteristics of the five types of filters. The ideal response is shown by dashed curves, while the solid lines indicate the practical filter response. A low-pass filter has a constant gain from 0 Hz to a high cutoff frequency f_H . Therefore, the bandwidth is also f_H . At f_H the gain is down by 3 dB; after that ($f > f_H$) it decreases with the increase in input frequency. The frequencies between 0 Hz and f_H are known as the passband frequencies, whereas the range of frequencies, those beyond f_H , that are attenuated includes the stopband frequencies.

Figure 8-1(a) shows the frequency response of the low-pass filter. As indicated by the dashed line, an *ideal* filter has a zero loss in its passband and infinite loss in its stopband. Unfortunately, ideal filter response is not practical because linear networks cannot produce the discontinuities. However, it is possible to obtain a practical response that approximates the ideal response by using special

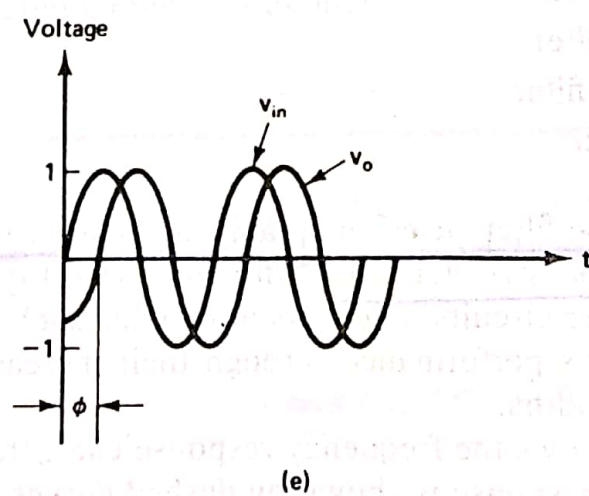
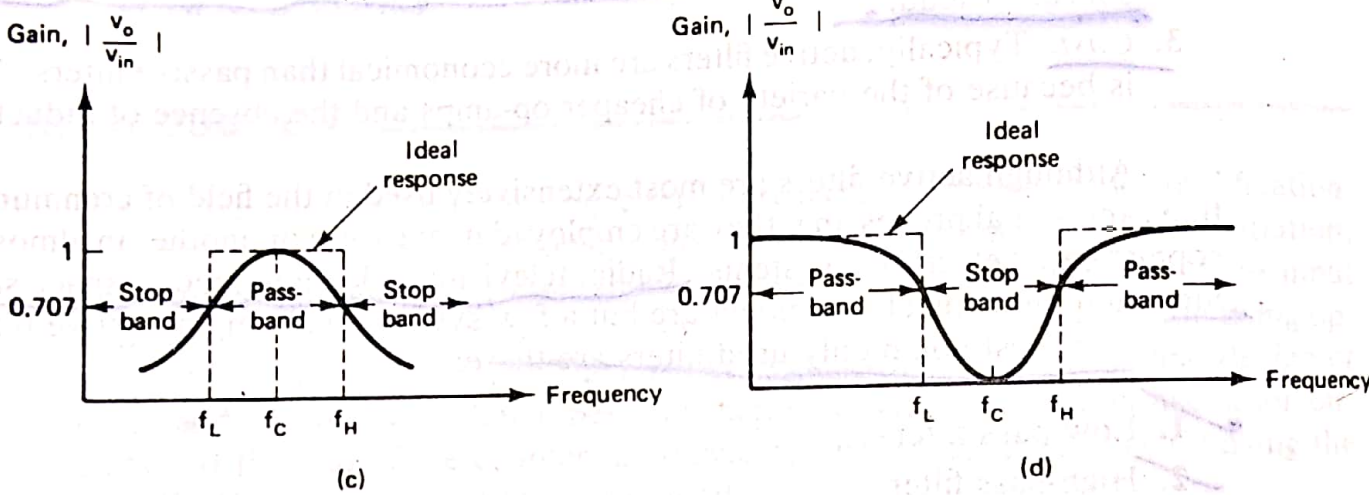
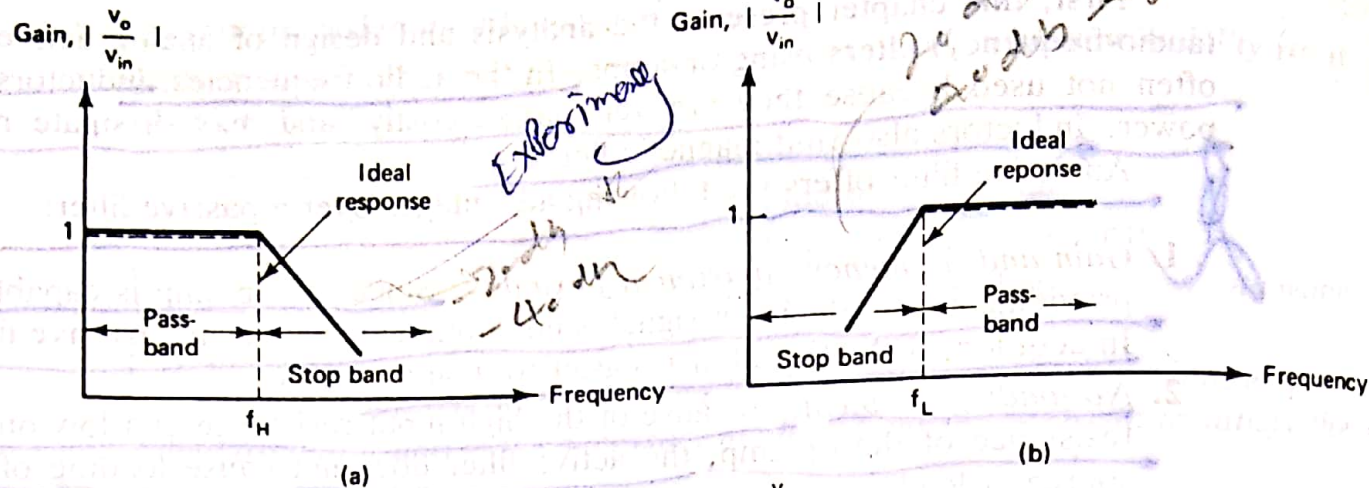


Figure 8-1 Frequency response of the major active filters. (a) Low pass. (b) High pass. (c) Band pass. (d) Band reject. (e) Phase shift between input and output voltages of an all-pass filter.

design techniques, as well as precision component values and high-speed op-amps.

Butterworth, Chebyshev, and Cauer filters are some of the most commonly used practical filters that approximate the ideal response. The key characteristic of the Butterworth filter is that it has a flat passband as well as stopband. For this reason, it is sometimes called a flat-flat filter. The Chebyshev filter has a ripple

passband and flat stopband, while the Cauer filter has a ripple passband and a ripple stopband. Generally, the Cauer filter gives the best stopband response among the three. Because of their simplicity of design, the low-pass and high-pass Butterworth filters are discussed here.

Figure 8-1(b) shows a high-pass filter with a stopband $0 < f < f_L$ and a passband $f > f_L$. f_L is the low cutoff frequency, and f is the operating frequency. A band-pass filter has a passband between two cutoff frequencies f_H and f_L , where $f_H > f_L$, and two stop-bands: $0 < f < f_L$ and $f > f_H$. The bandwidth of the band-pass filter, therefore, is equal to $f_H - f_L$. The band-reject filter performs exactly opposite to the band-pass; that is, it has a bandstop between two cutoff frequencies f_H and f_L and two passbands: $0 < f < f_L$ and $f > f_H$. The band-reject is also called a *band-stop* or *band-elimination* filter. The frequency responses of band-pass and band-reject filters are shown in Figure 8-1(c) and (d), respectively. In these figures, f_C is called the center frequency since it is approximately at the center of the passband or stopband.

Figure 8-1(e) shows the phase shift between input and output voltages of an all-pass filter. This filter passes all frequencies equally well; that is, output and input voltages are equal in amplitude for all frequencies, with the phase shift between the two a function of frequency. The highest frequency up to which the input and output amplitudes remain equal is dependent on the unity gain-bandwidth of the op-amp. At this frequency, however, the phase shift between the input and output is maximum.

Before proceeding with specific filter types, let us reexamine the filter characteristics, especially in the stopband region. As shown in Figure 8-1(a)–(d), the actual response curves of the filters in the stopband either steadily decrease or increase or both with increase in frequency. The rate at which the gain of the filter changes in the stopband is determined by the order of the filter. For example, for the first-order low-pass filter the gain rolls off at the rate of 20 dB/decade in the stopband, that is, for $f > f_H$; on the other hand, for the second-order low-pass filter the roll-off rate is 40 dB/decade; and so on. By contrast, for the first-order high-pass filter the gain increases at the rate of 20 dB/decade in the stopband, that is, until $f = f_L$; the increase is 40 dB/decade for the second-order high-pass filter; and so on.

8-3 FIRST-ORDER LOW-PASS BUTTERWORTH FILTER

Figure 8-2 shows a first-order low-pass Butterworth filter that uses an RC network for filtering. Note that the op-amp is used in the noninverting configuration; hence it does not load down the RC network. Resistors R_1 and R_F determine the gain of the filter.

According to the voltage-divider rule, the voltage at the noninverting terminal (across capacitor C) is

$$v_1 = \frac{-jX_C}{R - jX_C} v_{in} \quad (8-1a)$$

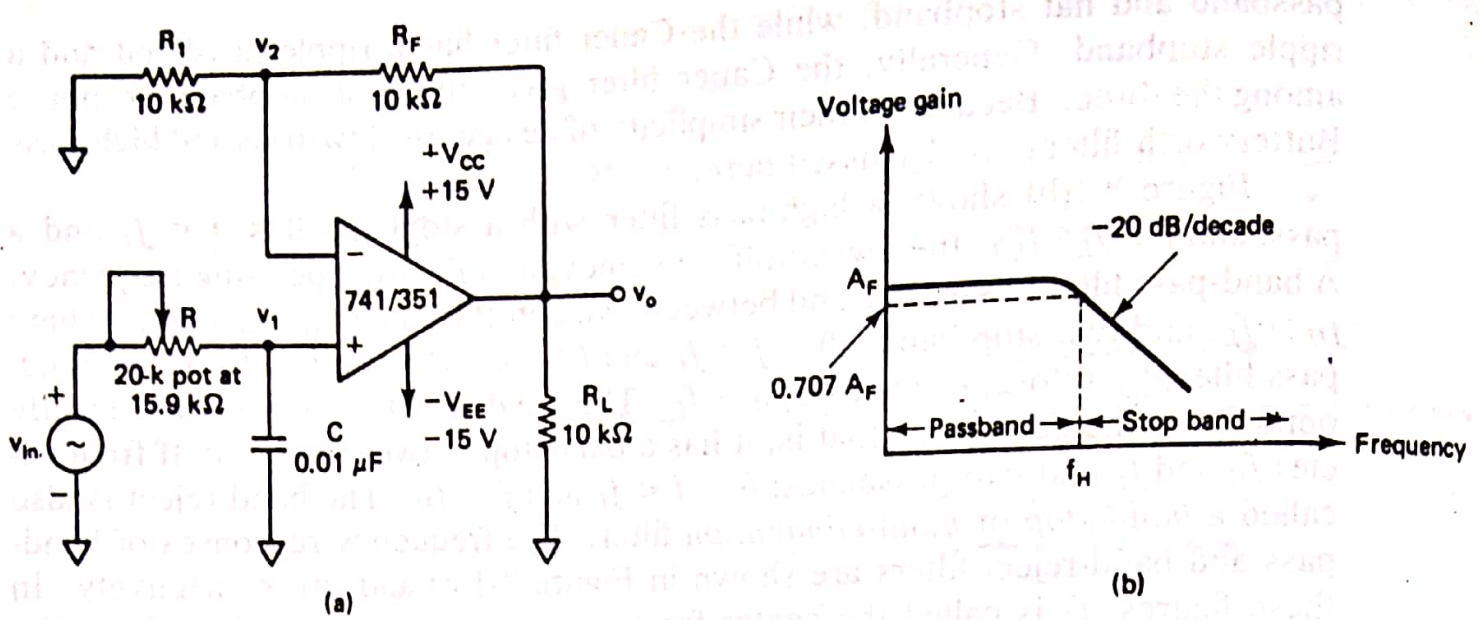


Figure 8-2 First-order low-pass Butterworth filter. (a) Circuit. (b) Frequency response.

where

$$j = \sqrt{-1} \quad \text{and} \quad -jX_C = \frac{1}{j2\pi fC}$$

Simplifying Equation (8-1a), we get

$$v_1 = \frac{v_{in}}{1 + j2\pi fRC}$$

and the output voltage

$$v_o = \left(1 + \frac{R_F}{R_1}\right) v_1$$

That is,

$$v_o = \left(1 + \frac{R_F}{R_1}\right) \frac{v_{in}}{1 + j2\pi fRC}$$

or

$$\frac{v_o}{v_{in}} = \frac{A_F}{1 + j(f/f_H)} \quad (8-1b)$$

where $\frac{v_o}{v_{in}}$ = gain of the filter as a function of frequency

$A_F = 1 + \frac{R_F}{R_1}$ = passband gain of the filter

f = frequency of the input signal

$f_H = \frac{1}{2\pi RC}$ = high cutoff frequency of the filter

The gain magnitude and phase angle equations of the low-pass filter can be obtained by converting Equation (8-1b) into its equivalent polar form, as follows:

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + (f/f_H)^2}} \quad (8-2a)$$

$$\phi = -\tan^{-1} \left(\frac{f}{f_H} \right) \quad (8-2b)$$

where ϕ is the phase angle in degrees.

The operation of the low-pass filter can be verified from the gain magnitude equation, (8-2a):

1. At very low frequencies, that is, $f < f_H$,

$$\left| \frac{V_o}{V_{in}} \right| \cong A_F$$

2. At $f = f_H$,

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{2}} = 0.707A_F$$

3. At $f > f_H$,

$$\left| \frac{V_o}{V_{in}} \right| < A_F$$

Thus the low-pass filter has a constant gain A_F from 0 Hz to the high cutoff frequency f_H . At f_H the gain is $0.707A_F$, and after f_H it decreases at a constant rate with an increase in frequency [see Figure 8-2(b)]. That is, when the frequency is increased tenfold (one decade), the voltage gain is divided by 10. In other words, the gain decreases 20 dB ($= 20 \log 10$) each time the frequency is increased by 10. Hence the rate at which the gain rolls off after f_H is 20 dB/decade or 6 dB/octave, where octave signifies a twofold increase in frequency. The frequency $f = f_H$ is called the cutoff frequency because the gain of the filter at this frequency is down by 3 dB ($= 20 \log 0.707$) from 0 Hz. Other equivalent terms for cutoff frequency are -3 dB frequency, break frequency, or corner frequency.

8-3.1 Filter Design

A low-pass filter can be designed by implementing the following steps:

1. Choose a value of high cutoff frequency f_H .
2. Select a value of C less than or equal to $1 \mu\text{F}$. Mylar or tantalum capacitors are recommended for better performance.
3. Calculate the value of R using

$$R = \frac{1}{2\pi f_H C}$$

4. Finally, select values of R_1 and R_F dependent on the desired passband gain A_F using

$$A_F = 1 + \frac{R_F}{R_1}$$

8-3.2 Frequency Scaling

Once a filter is designed, there may sometimes be a need to change its cutoff frequency. The procedure used to convert an original cutoff frequency f_H to a new cutoff frequency f'_H is called *frequency scaling*. Frequency scaling is accomplished as follows. To change a high cutoff frequency, multiply R or C , but not both, by the ratio of the original cutoff frequency to the new cutoff frequency. In filter design the needed values of R and C are often not standard. Besides, a variable capacitor C is not commonly used. Therefore, choose a standard value of capacitor, and then calculate the value of resistor for a desired cutoff frequency. This is because for a nonstandard value of resistor a potentiometer can be used (see Examples 8-1 and 8-2).

EXAMPLE 8-1

Design a low-pass filter at a cutoff frequency of 1 kHz with a passband gain of 2.

SOLUTION Follow the preceding design steps.

1. $f_H = 1$ kHz.
2. Let $C = 0.01$ μF .
3. Then $R = 1/(2\pi)(10^3)(10^{-8}) = 15.9$ k Ω . (Use a 20-k Ω potentiometer.)
4. Since the passband gain is 2, R_1 and R_F must be equal. Therefore, let $R_1 = R_F = 10$ k Ω . The complete circuit with component values is shown in Figure 8-2(a).

EXAMPLE 8-2

Using the frequency scaling technique, convert the 1-kHz cutoff frequency of the low-pass filter of Example 8-1 to a cutoff frequency of 1.6 kHz.

SOLUTION To change a cutoff frequency from 1 kHz to 1.6 kHz, we multiply the 15.9-k Ω resistor by

$$\frac{\text{original cutoff frequency}}{\text{new cutoff frequency}} = \frac{1 \text{ kHz}}{1.6 \text{ kHz}} = 0.625$$

Therefore, new resistor $R = (15.9 \text{ k}\Omega)(0.625) = 9.94 \text{ k}\Omega$. However, $9.94 \text{ k}\Omega$ is not a standard value. Therefore, use $R = 10 \text{ k}\Omega$ potentiometer and adjust it to $9.94 \text{ k}\Omega$. Thus the new cutoff frequency is

$$f_H = \frac{1}{(2\pi)(0.01 \mu\text{F})(9.94 \text{ k}\Omega)}$$

$$= 1.6 \text{ kHz}$$

EXAMPLE 8-3

Plot the frequency response of the low-pass filter of Example 8-1.

SOLUTION To plot the frequency response, we have to use Equation (8-2a). The data of Table 8-1 are, therefore, obtained by substituting various values for f in this equation. Equation (8-2a) will be repeated here for convenience:

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_F}{\sqrt{1 + (f/f_H)^2}}$$

where $A_F = 2$ and $f_H = 1 \text{ kHz}$. The data of Table 8-1 are plotted as shown in Figure 8-3.

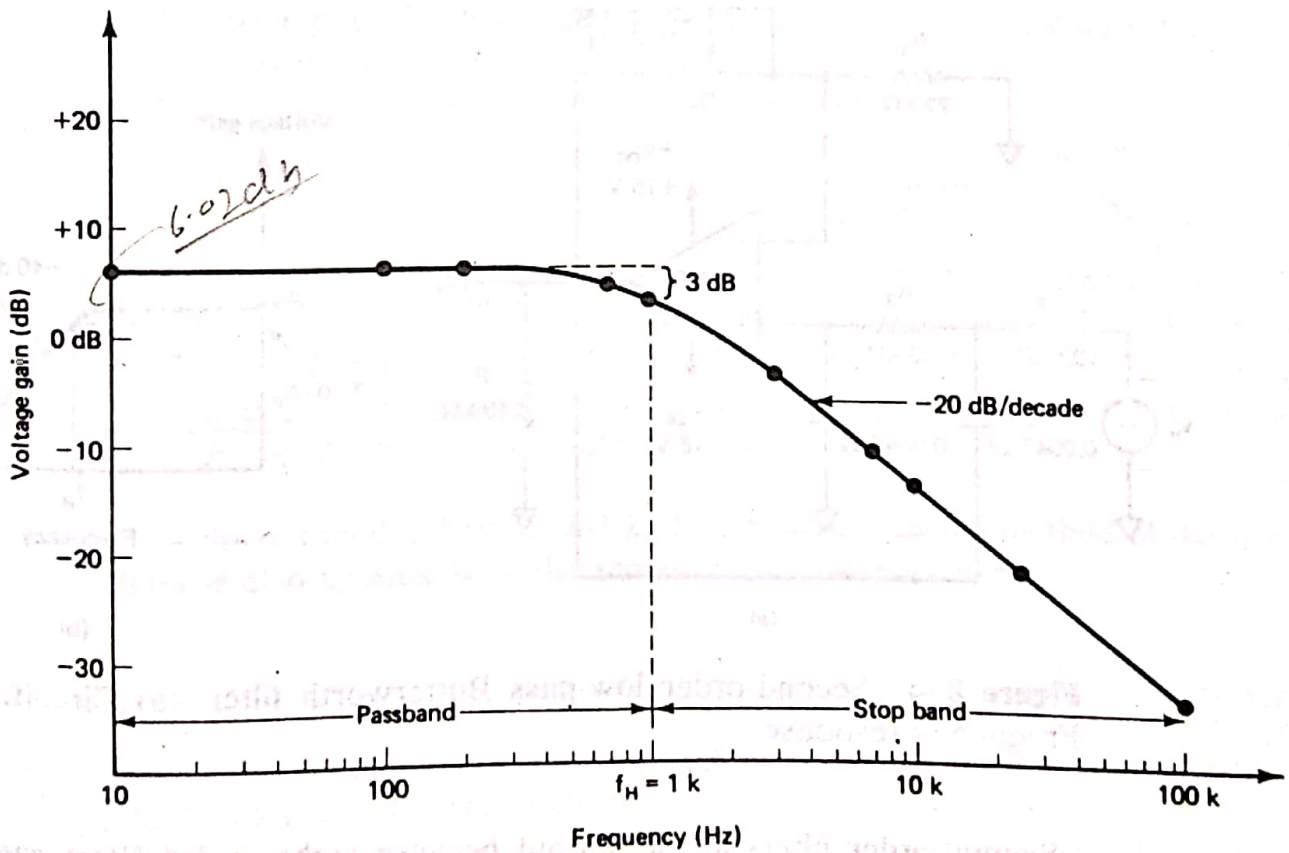


Figure 8-3 Frequency response for Example 8-3.

TABLE 8-1 FREQUENCY RESPONSE DATA FOR EXAMPLE 8-3

Input frequency, f (Hz)	Gain magnitude, $ v_o/v_{in} $	Magnitude (dB) = $20 \log v_o/v_{in} $
10	2	6.02
100	1.99	5.98
200	1.96	5.85
700	1.64	4.29
1,000	1.41	3.01
3,000	0.63	-3.98
7,000	0.28	-10.97
10,000	0.20	-14.02
30,000	0.07	-23.53
100,000	0.02	-33.98

8-4 SECOND-ORDER LOW-PASS BUTTERWORTH FILTER

A stop-band response having a 40-dB/decade roll-off is obtained with the second-order low-pass filter. A first-order low-pass filter can be converted into a second-order type simply by using an additional RC network, as shown in Figure 8-4.

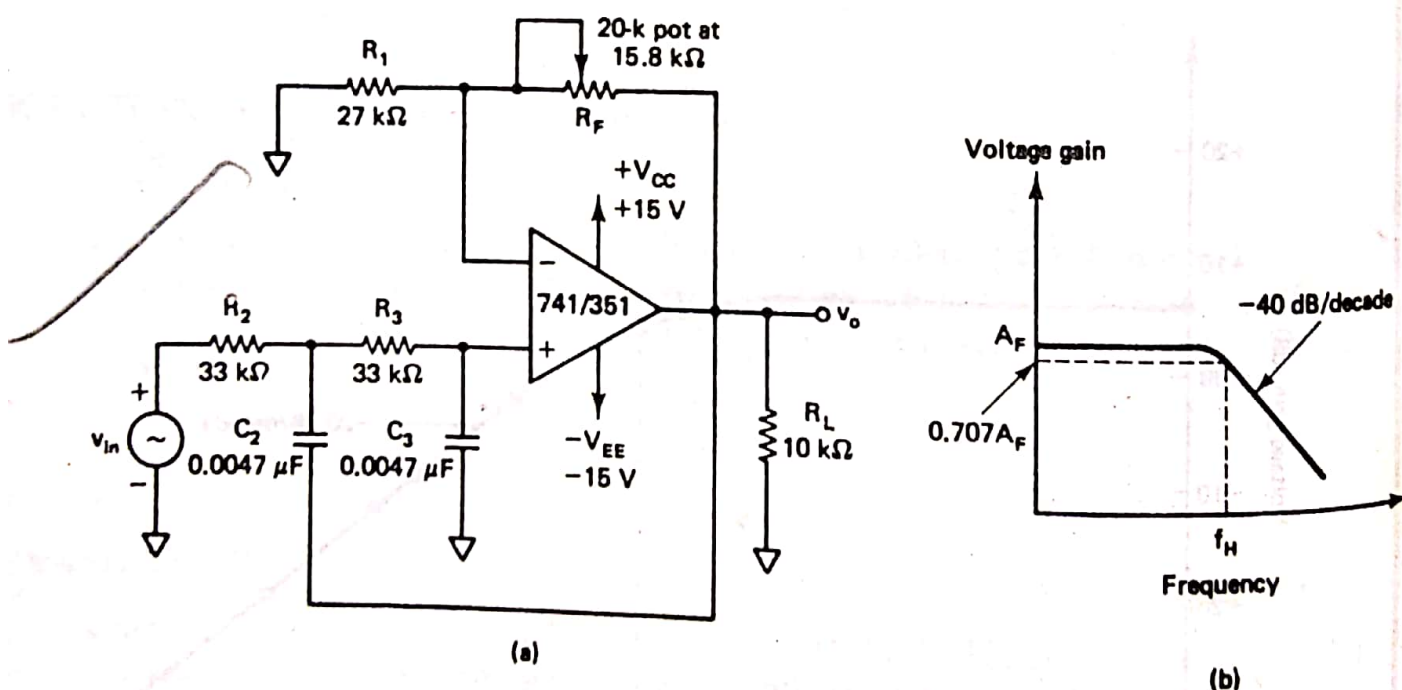


Figure 8-4 Second-order low-pass Butterworth filter. (a) Circuit. (b) Frequency response.

Second-order filters are important because higher-order filters can be designed using them. The gain of the second-order filter is set by R_1 and R_F , while the high cutoff frequency f_H is determined by R_2 , C_2 , R_3 , and C_3 , as follows:

$$f_H = \frac{1}{2\pi\sqrt{R_2R_3C_2C_3}} \quad (8-3)$$

For the derivation of f_H , refer to Appendix C.

Furthermore, for a second-order low-pass Butterworth response, the voltage gain magnitude equation is

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_F}{\sqrt{1 + (f/f_H)^4}} \quad (8-4)$$

where $A_F = 1 + \frac{R_F}{R_1}$ = passband gain of the filter

f = frequency of the input signal (Hz)

$$f_H = \frac{1}{2\pi\sqrt{R_2R_3C_2C_3}} = \text{high cutoff frequency (Hz)}$$

8-4.1 Filter Design

Except for having twice the roll-off rate in the stopband, the frequency response of the second-order low-pass filter is identical to that of the first-order type. Therefore, the design steps of the second-order filter are identical to those of the first-order filter, as follows:

1. Choose a value for the high cutoff frequency f_H .
2. To simplify the design calculations, set $R_2 = R_3 = R$ and $C_2 = C_3 = C$. Then choose a value of $C \leq 1 \mu\text{F}$.
3. Calculate the value of R using Equation (8-3):

$$R = \frac{1}{2\pi f_H C}$$

4. Finally, because of the equal resistor ($R_2 = R_3$) and capacitor ($C_2 = C_3$) values, the passband voltage gain $A_F = (1 + R_F/R_1)$ of the second-order low-pass filter has to be equal to 1.586. That is, $R_F = 0.586R_1$. This gain is necessary to guarantee Butterworth response. Hence choose a value of $R_1 \leq 100 \text{ k}\Omega$ and calculate the value of R_F .

As outlined in Section 8-3.2, the frequency scaling method of the first-order filter is also applicable to the second-order low-pass filter.

EXAMPLE 8-4

- (a) Design a second-order low-pass filter at a high cutoff frequency of 1 kHz.
- (b) Draw the frequency response of the network in part (a).

SOLUTION (a) To design the second-order low-pass filter, simply follow the steps just presented:

1. $f_H = 1 \text{ kHz}$.
2. Let $C_2 = C_3 = 0.0047 \mu\text{F}$.
3. Then

$$R_2 = R_3 = \frac{1}{(2\pi)(10^3)(47)(10^{-10})} = 33.86 \text{ k}\Omega$$

(Use $R_2 = R_3 = 33 \text{ k}\Omega$.)

4. Since R_F must be equal to $0.586R_1$, let R_1 equal $27 \text{ k}\Omega$. Therefore,

$$R_F = (0.586)(27 \text{ k}\Omega) = 15.82 \text{ k}\Omega$$

(Use $R_F = 20 \text{ k}\Omega$ pot.) Thus the required components are

$$R_2 = R_3 = 33 \text{ k}\Omega$$

$$C_2 = C_3 = 0.0047 \mu\text{F}$$

$$R_1 = 27 \text{ k}\Omega \quad \text{and} \quad R_F = 15.8 \text{ k}\Omega \text{ (20k } - \Omega \text{ pot)}$$

Another method to design the second-order low-pass filter is to use the same values of resistor and capacitor obtained for the first-order filter in Example 8-1. This is because the cutoff frequency of both the second-order and first-order filters is 1 kHz . Therefore, we may use $R_2 = R_3 = 15.9 \text{ k}\Omega$ and $C_2 = C_3 = 0.01 \mu\text{F}$. However, the values of R_1 and R_F must be chosen such that $R_F = 0.586R_1$. Therefore, use $R_1 = 27 \text{ k}\Omega$ and $R_F = 15.8 \text{ k}\Omega$.

(b) The frequency response data shown in Table 8-2 are obtained from the magnitude equation, (8-4), by substituting various values from 10 Hz to 100 kHz for f . Equation (8-4) is repeated here for convenience:

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_F}{\sqrt{1 + (f/f_H)^4}}$$

where $A_F = 1.586$ and $f_H = 1 \text{ kHz}$. The frequency response of the second-order low-pass filter of Example 8-4 is shown in Figure 8-5.

TABLE 8-2 FREQUENCY RESPONSE DATA FOR EXAMPLE 8-4

Frequency, f (Hz)	Gain magnitude, $ v_o/v_{in} $	Magnitude (dB) = $20 \log v_o/v_{in} $
10	1.59	4.01
100	1.59	4.01
200	1.58	4.00
700	1.42	3.07
1,000	1.12	1.00
3,000	0.18	-15.13
7,000	0.03	-29.80
10,000	0.02	-35.99
30,000	1.76×10^{-3}	-55.08
100,000	1.59×10^{-4}	-75.99

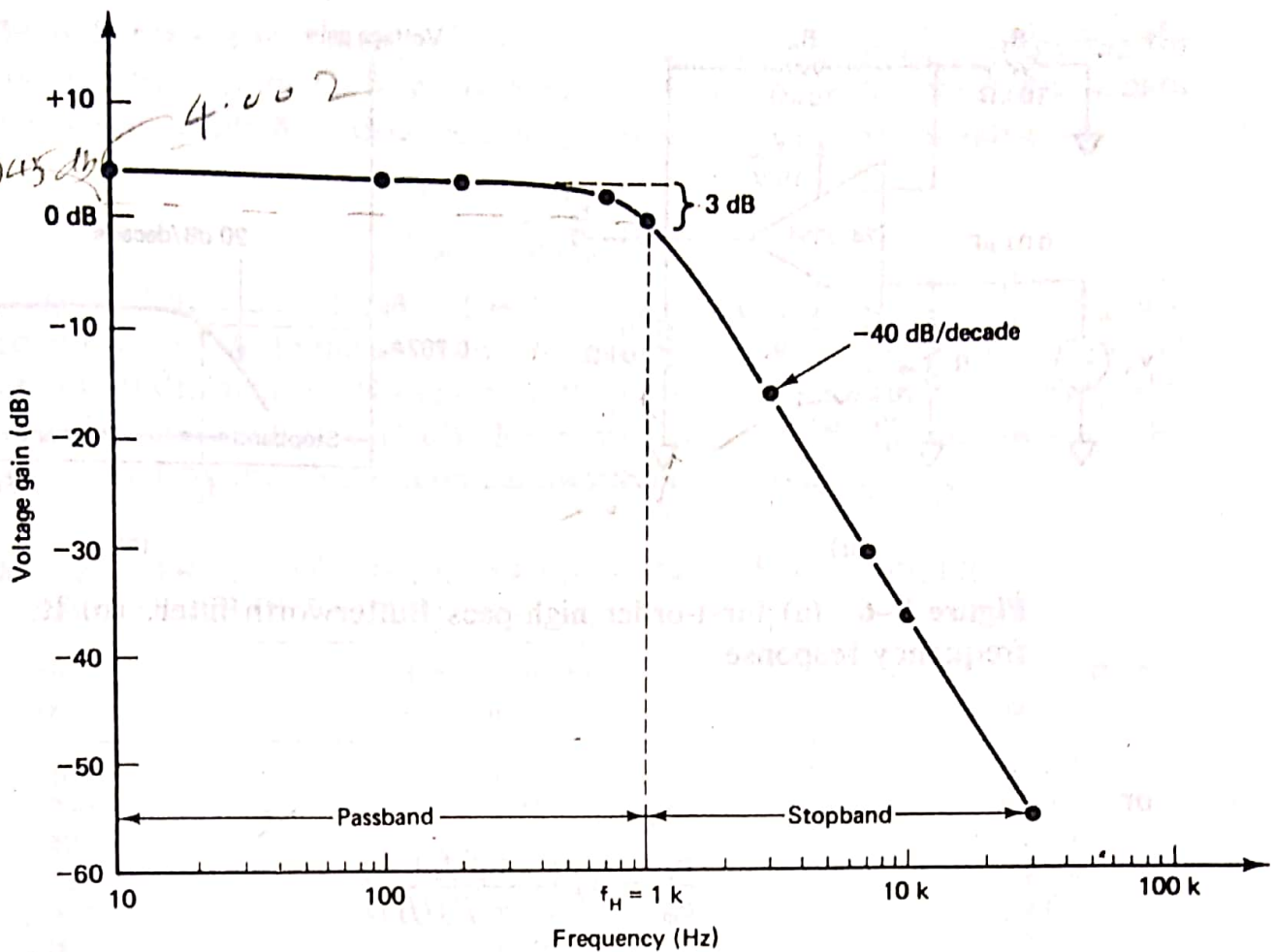


Figure 8-5 Frequency response for Example 8-4.



8-5 FIRST-ORDER HIGH-PASS BUTTERWORTH FILTER

High-pass filters are often formed simply by interchanging frequency-determining resistors and capacitors in low-pass filters. That is, a first-order high-pass filter is formed from a first-order low-pass type by interchanging components R and C . Similarly, a second-order high-pass filter is obtained from a second-order low-pass filter if R and C are interchanged, and so on. Figure 8-6 shows a first-order high-pass Butterworth filter with a low cutoff frequency of f_L . This is the frequency at which the magnitude of the gain is 0.707 times its passband value. Obviously, all frequencies higher than f_L are passband frequencies, with the highest frequency determined by the closed-loop bandwidth of the op-amp.

Note that the high-pass filter of Figure 8-6(a) and the low-pass filter of Figure 8-2(a) are the same circuits, except that the frequency-determining components (R and C) are interchanged.

For the first-order high-pass filter of Figure 8-6(a), the output voltage is
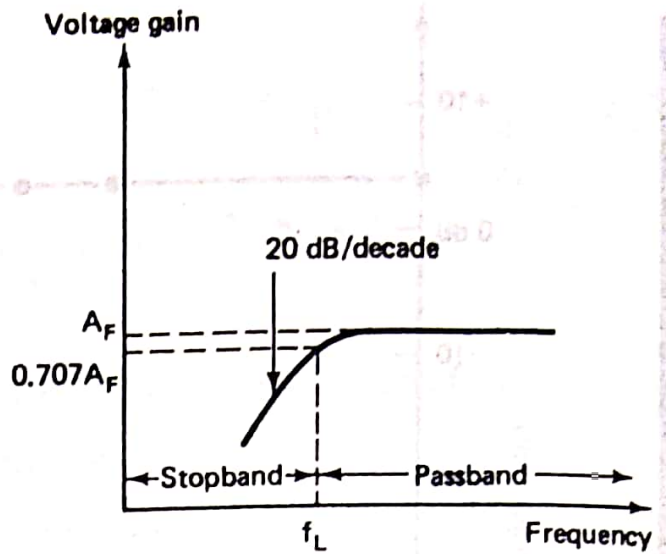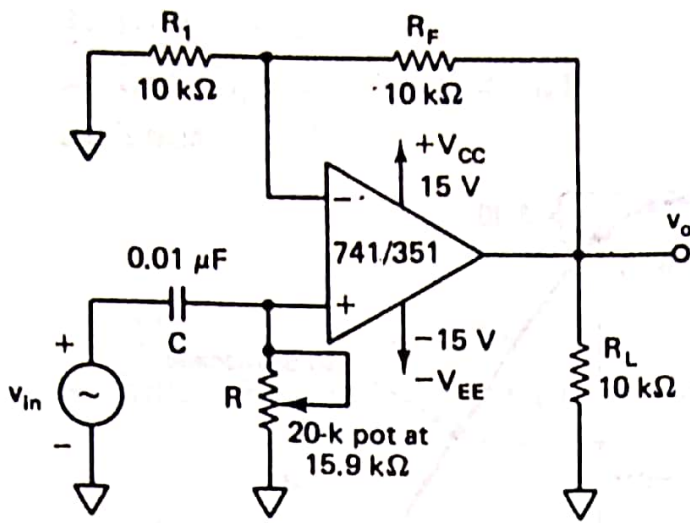
$$v_o = \left(1 + \frac{R_F}{R_1}\right) \frac{j2\pi fRC}{1 + j2\pi fRC} v_{in}$$



(a) (b)

Figure 8-6 (a) First-order high-pass Butterworth filter. (b) Its frequency response.

or

$$\frac{v_o}{v_{in}} = A_F \left[\frac{j(f/f_L)}{1 + j(f/f_L)} \right] \quad (8-5)$$

where $A_F = 1 + \frac{R_F}{R_1}$ = passband gain of the filter

f = frequency of the input signal (Hz)

$$f_L = \frac{1}{2\pi RC} = \text{low cutoff frequency (Hz)}$$

Hence the magnitude of the voltage gain is

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_F(f/f_L)}{\sqrt{1 + (f/f_L)^2}} \quad (8-6)$$

Since high-pass filters are formed from low-pass filters simply by interchanging R 's and C 's, the design and frequency scaling procedures of the low-pass filters are also applicable to the high-pass filters (see Sections 8-3.1 and 8-3.2).

8-6 SECOND-ORDER HIGH-PASS BUTTERWORTH FILTER

As in the case of the first-order filter, a second-order high-pass filter can be formed from a second-order low-pass filter simply by interchanging the frequency-determining resistors and capacitors. Figure 8-8(a) shows the second-order high-pass filter.

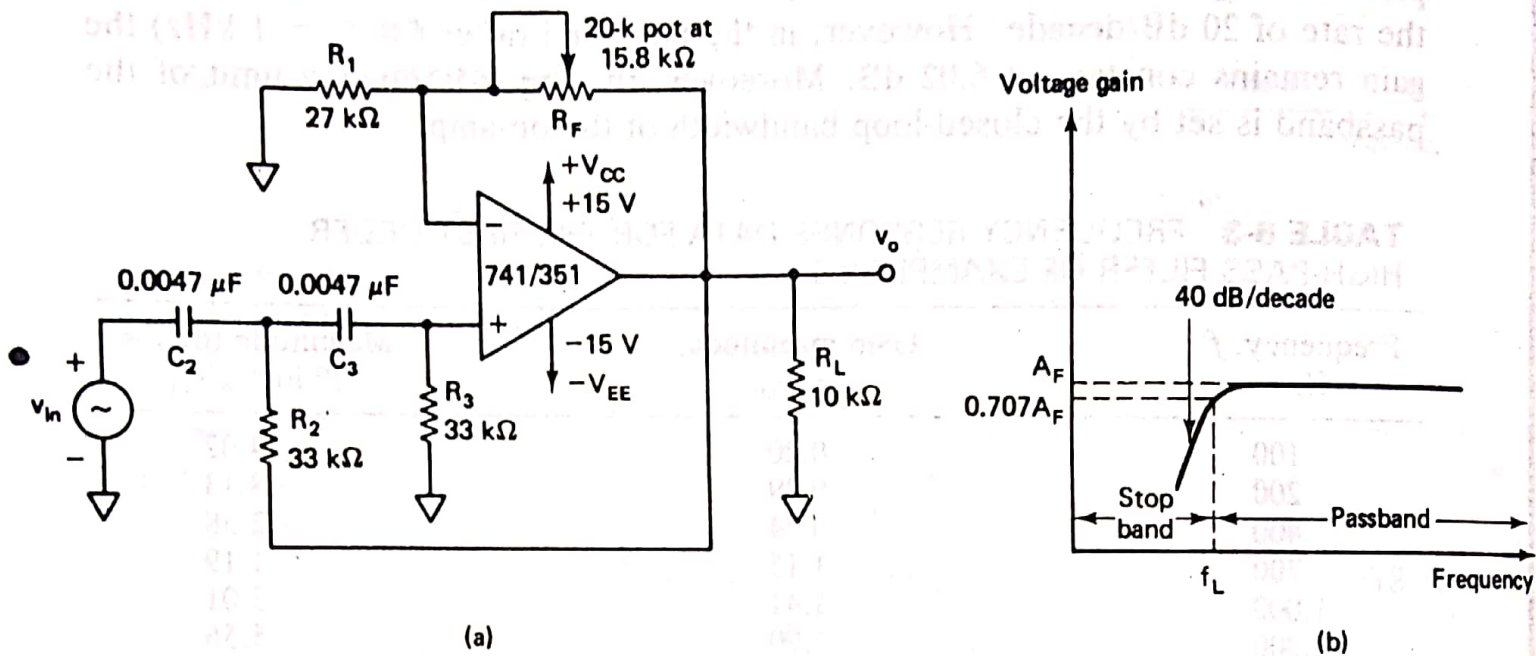


Figure 8-8 (a) Second-order high-pass Butterworth filter. (b) Its frequency response.

The voltage gain magnitude equation of the second-order high-pass filter is as follows:

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_F}{\sqrt{1 + (f_L/f)^4}} \quad (8-7)$$

where $A_F = 1.586$ = passband gain for the second-order Butterworth response
 f = frequency of the input signal (Hz)
 f_L = low cutoff frequency (Hz)

Since second-order low-pass and high-pass filters are the same circuits except that the positions of resistors and capacitors are interchanged, the design and frequency scaling procedures for the high-pass filter are the same as those for the low-pass filter.

EXAMPLE 8-6

- Determine the low cutoff frequency f_L of the filter shown in Figure 8-8(a).
- Draw the frequency response plot of the filter.

SOLUTION (a)

$$f_L = \frac{1}{2\pi \sqrt{R_2 R_3 C_2 C_3}}$$

$$= \frac{1}{2\pi \sqrt{(33 \text{ k}\Omega)^2 (0.0047 \text{ }\mu\text{F})^2}} \cong 1 \text{ kHz}$$

(b) The frequency response data in Table 8-4 are obtained from the voltage gain magnitude equation, (8-7), which is repeated here for convenience:

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_F}{\sqrt{1 + (f_L/f)^4}}$$

where $A_F = 1.586$ and $f_L = 1 \text{ kHz}$. The resulting frequency response plot is shown in Figure 8-9.

TABLE 8-4 FREQUENCY RESPONSE DATA FOR SECOND-ORDER HIGH-PASS FILTER OF EXAMPLE 8-6

Input frequency, $f(\text{Hz})$	Gain magnitude, $ v_o/v_{in} $	Magnitude (dB) = $20 \log v_o/v_{in} $
100	0.01586	-35.99
200	0.0634	-23.96
700	0.6979	-3.124
1,000	1.1215	0.9960
3,000	1.5763	3.953
7,000	1.5857	4.004
10,000	1.5859	4.006
30,000	1.5860	4.006
100,000	1.5860	4.006

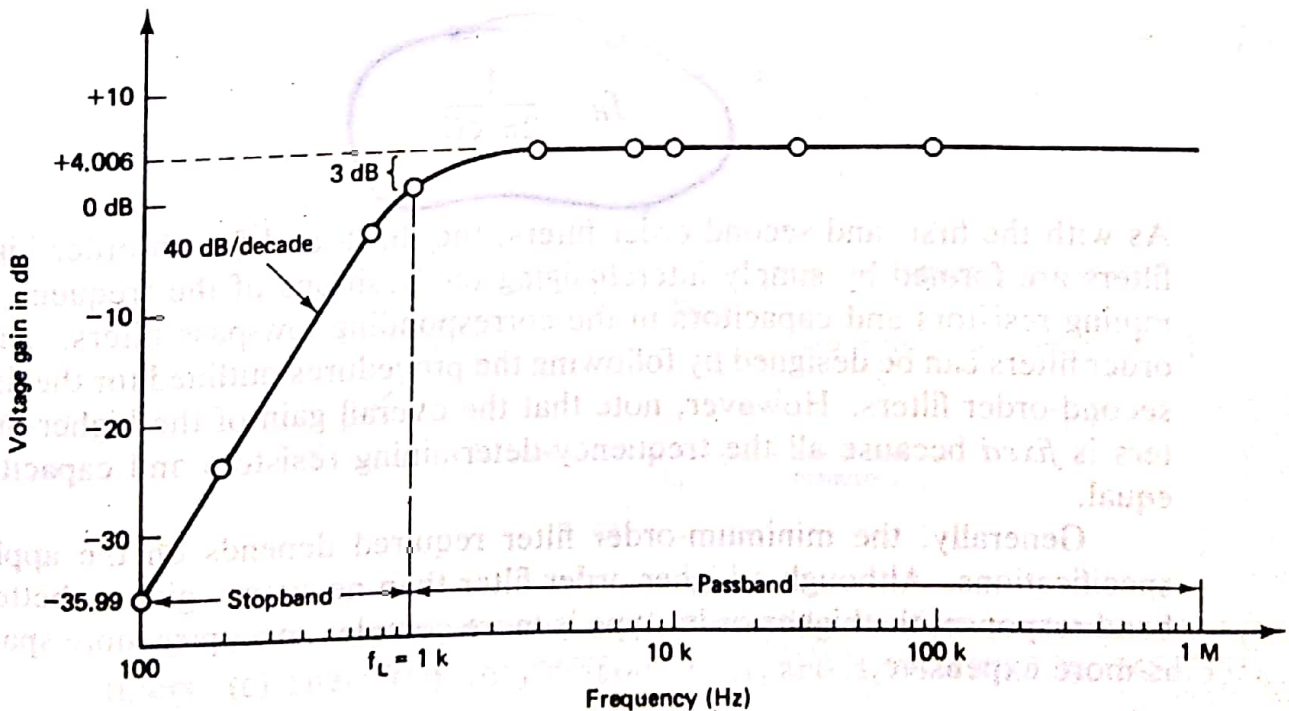


Figure 8-9 Frequency response for Example 8-6.

8-7 HIGHER-ORDER FILTERS

From the preceding discussions of filters we can conclude that in the stopband the gain of the filter changes at the rate of 20 dB/decade for first-order filters and at 40 dB/decade for second-order filters. This means that, as the order of the filter is increased, the actual stopband response of the filter approaches its ideal stopband characteristic.


Higher-order filters, such as third, fourth, fifth, and so on, are formed simply by using the first- and second-order filters. For example, a third-order low-pass filter is formed by connecting in series or cascading first- and second-order low-pass filters; a fourth-order low-pass filter is composed of two cascaded second-order low-pass sections, and so on. Although there is no limit to the order of the filter that can be formed, as the order of the filter increases, so does its size. Also, its accuracy declines, in that the difference between the actual stopband response and the theoretical stopband response increases with an increase in the order of the filter. Figure 8-10 shows third- and fourth-order low-pass Butterworth filters. Note that in the third-order filter the voltage gain of the first-order section is *one*, and that of the second-order section is *two*. On the other hand, in the fourth-order filter the gain of the first section is 1.152, while that of the second section is 2.235. These gain values are necessary to guarantee Butterworth response and have to remain the same regardless of the filter's cutoff frequency. Furthermore, the overall gain of the filter is equal to the product of the individual voltage gains of the filter sections. Thus the overall gain of the third-order filters is 2.0, and that of the fourth order is $(1.152)(2.235) = 2.57$.

Since the frequency-determining resistors are equal and the frequency-determining capacitors are also equal, the high cutoff frequencies of the third- and fourth-order low-pass filters in Figure 8-10(a) and (b) must also be equal. That is,


$$f_H = \frac{1}{2\pi RC} \quad (8-8)$$

As with the first- and second-order filters, the third- and fourth-order high-pass filters are formed by simply interchanging the positions of the frequency-determining resistors and capacitors in the corresponding low-pass filters. The high-order filters can be designed by following the procedures outlined for the first- and second-order filters. However, note that the overall gain of the higher-order filter is *fixed* because all the frequency-determining resistors and capacitors are equal.

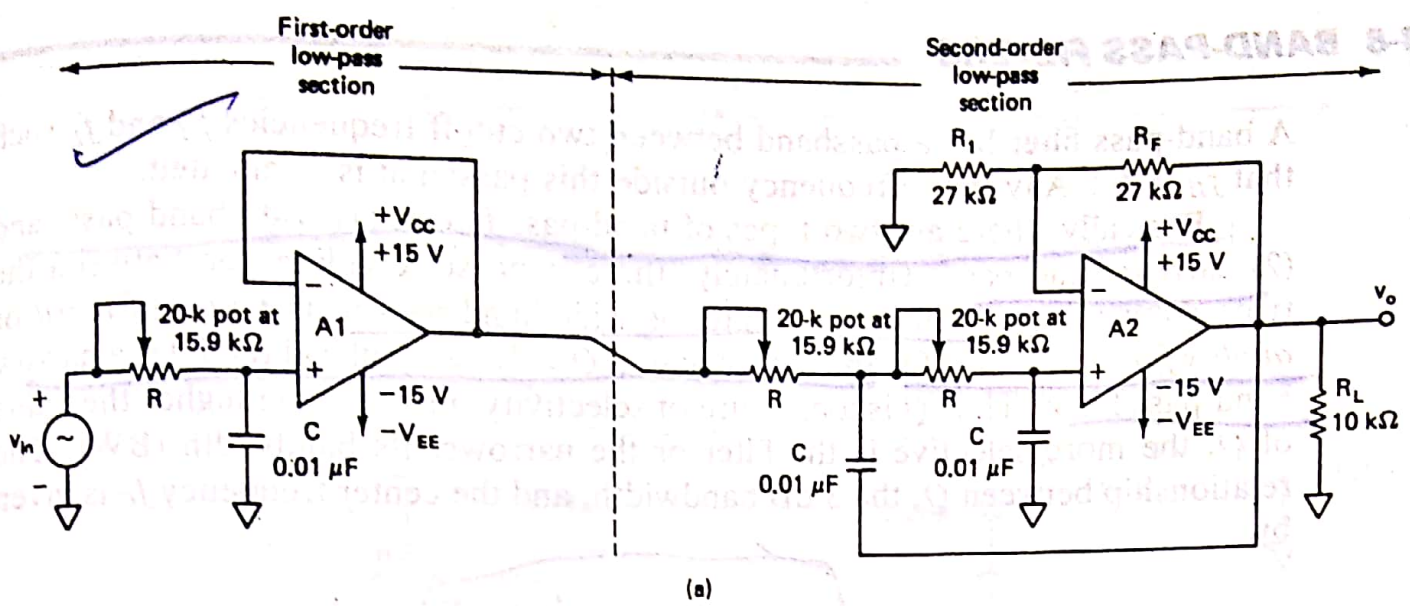Generally, the minimum-order filter required depends on the application specifications. Although a higher-order filter than necessary gives a better stopband response, the higher-order type is more complex, occupies more space, and is more expensive.




(a)

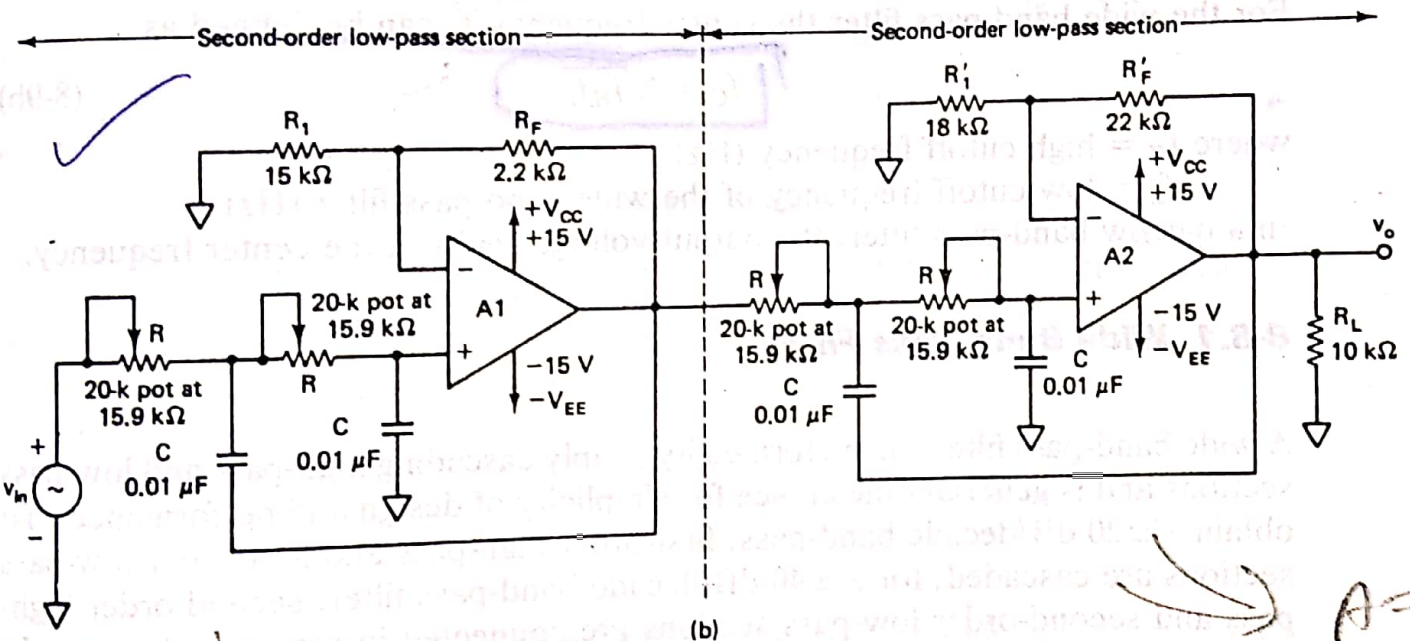

(b)

$A = 1.148$

$A = 2$

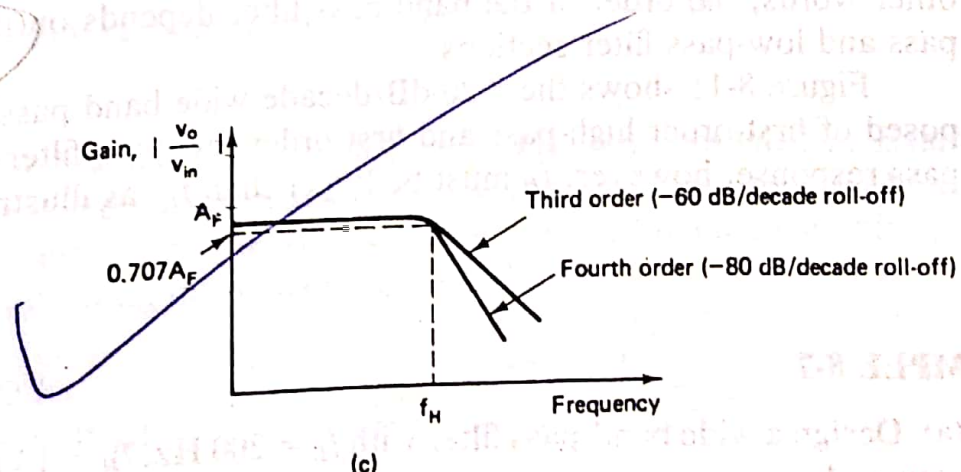

(c)

Figure 8-10 (a) Third-order and (b) fourth-order low-pass Butterworth filters. (c) Their frequency responses. A_1 and A_2 dual op-amp: 1458/353.

8-8 BAND-PASS FILTERS

A band-pass filter has a passband between two cutoff frequencies f_H and f_L , such that $f_H > f_L$. Any input frequency outside this passband is attenuated.

Basically, there are two types of band-pass filters: (1) wide band pass, and (2) narrow band pass. Unfortunately, there is no set dividing line between the two. However, we will define a filter as wide band pass if its figure of merit or quality factor $Q < 10$. On the other hand, if $Q > 10$, we will call the filter a narrow band-pass filter. Thus Q is a measure of selectivity, meaning the higher the value of Q , the more selective is the filter or the narrower its bandwidth (BW). The relationship between Q , the 3-dB bandwidth, and the center frequency f_c is given by

$$Q = \frac{f_c}{\text{BW}} = \frac{f_c}{f_H - f_L} \quad (8-9a)$$

For the wide band-pass filter the center frequency f_c can be defined as

$$f_c = \sqrt{f_H f_L} \quad (8-9b)$$

where f_H = high cutoff frequency (Hz)

f_L = low cutoff frequency of the wide band-pass filter (Hz)

In a narrow band-pass filter, the output voltage peaks at the center frequency.

8-8.1 Wide Band-Pass Filter

A wide band-pass filter can be formed by simply cascading high-pass and low-pass sections and is generally the choice for simplicity of design and performance. To obtain a ± 20 dB/decade band-pass, first-order high-pass and first-order low-pass sections are cascaded; for a ± 40 -dB/decade band-pass filter, second-order high-pass and second-order low-pass sections are connected in series, and so on. In other words, the order of the band-pass filter depends on the order of the high-pass and low-pass filter sections.

Figure 8-11 shows the ± 20 -dB/decade wide band-pass filter, which is composed of first-order high-pass and first-order low-pass filters. To realize a band-pass response, however, f_H must be larger than f_L , as illustrated in Example 8-7.

EXAMPLE 8-7

- Design a wide band-pass filter with $f_L = 200$ Hz, $f_H = 1$ kHz, and a passband gain = 4.
- Draw the frequency response plot of this filter.
- Calculate the value of Q for the filter.

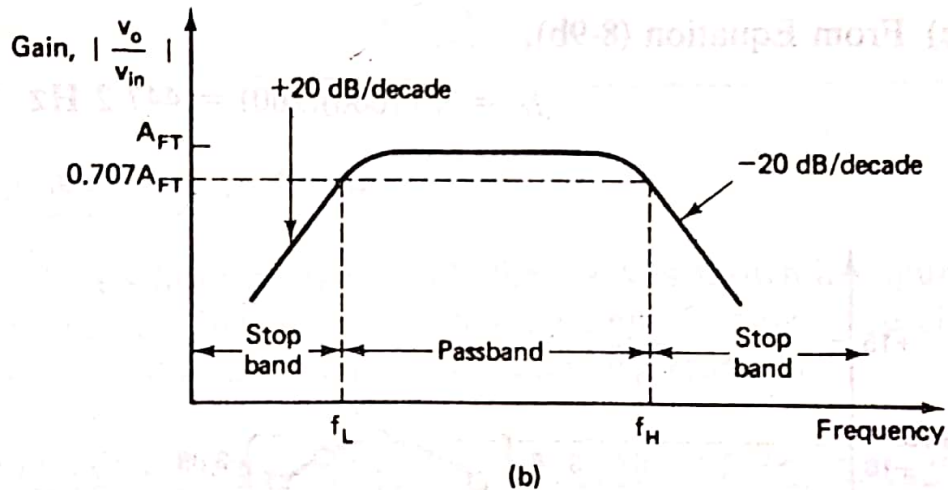
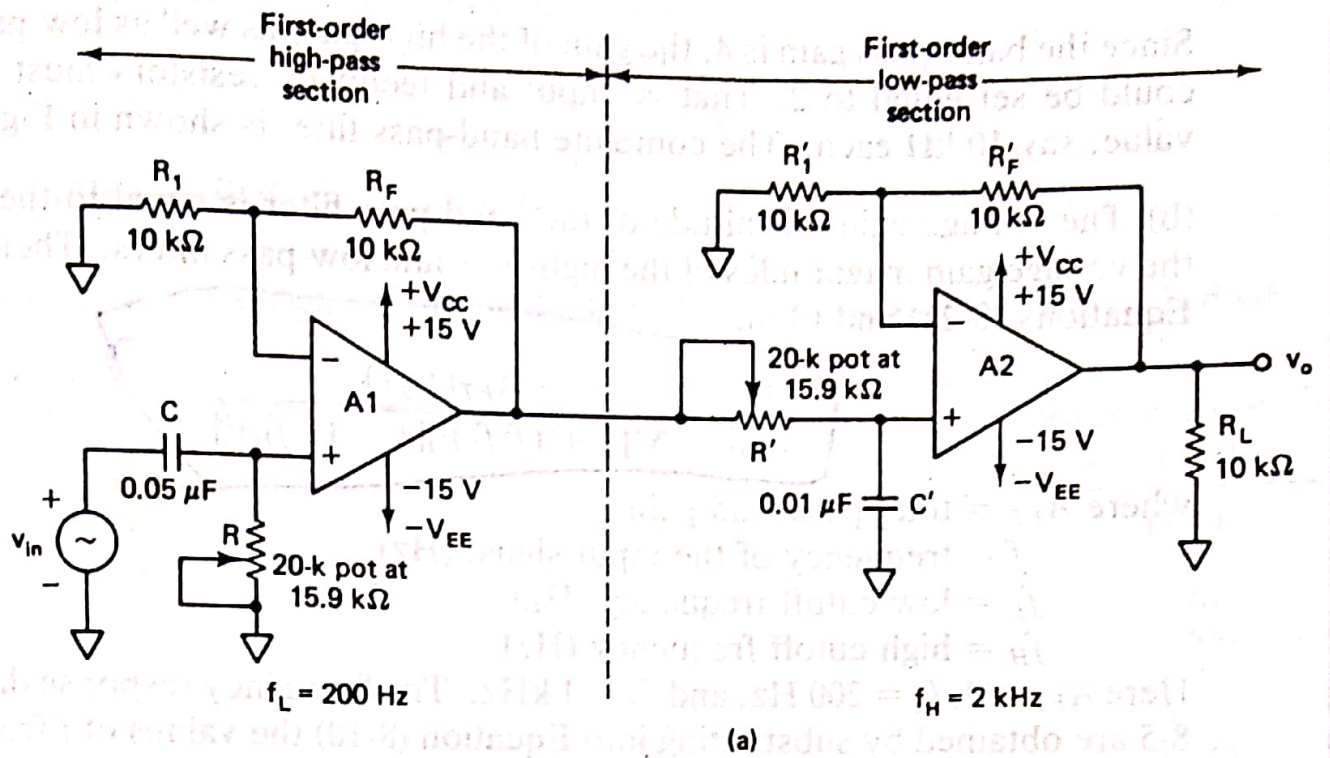


Figure 8-11 (a) ± 20 dB/decade-wide band-pass filter. (b) Its frequency response. A_1 and A_2 dual op-amp: 1458/353.

SOLUTION (a) A low-pass filter with $f_H = 1$ kHz was designed in Example 8-1; therefore, the same values of resistors and capacitors can be used here, that is, $R' = 15.9$ k Ω and $C' = 0.01$ μ F. As in the case of the high-pass filter, it can be designed by following the steps of Section 8-3.1:

1. $f_L = 200$ Hz.
2. Let $C = 0.05$ μ F.
3. Then

$$R = \frac{1}{2\pi f_L C} = \frac{1}{(2\pi)(200)(5)(10^{-8})} = 15.9 \text{ k}\Omega$$

Since the band-pass gain is 4, the gain of the high-pass as well as low-pass sections could be set equal to 2. That is, input and feedback resistors must be equal in value, say 10 kΩ each. The complete band-pass filter is shown in Figure 8-11(a).

(b) The voltage gain magnitude of the band-pass filter is equal to the product of the voltage gain magnitudes of the high-pass and low-pass filters. Therefore, from Equations (8-2a) and (8-6),

$$\left| \frac{v_o}{v_{in}} \right| = \frac{A_{FT}(f/f_L)}{\sqrt{[1 + (f/f_L)^2][1 + (f/f_H)^2]}} \quad (8-10)$$

- where A_{FT} = total passband gain
- f = frequency of the input signal (Hz)
- f_L = low cutoff frequency (Hz)
- f_H = high cutoff frequency (Hz)

Here $A_{FT} = 4$, $f_L = 200$ Hz, and $f_H = 1$ kHz. The frequency response data in Table 8-5 are obtained by substituting into Equation (8-10) the values of f from 10 Hz to 10 kHz. The frequency response plot is shown in Figure 8-12.

(c) From Equation (8-9b),

$$f_c = \sqrt{(1000)(200)} = 447.2 \text{ Hz}$$

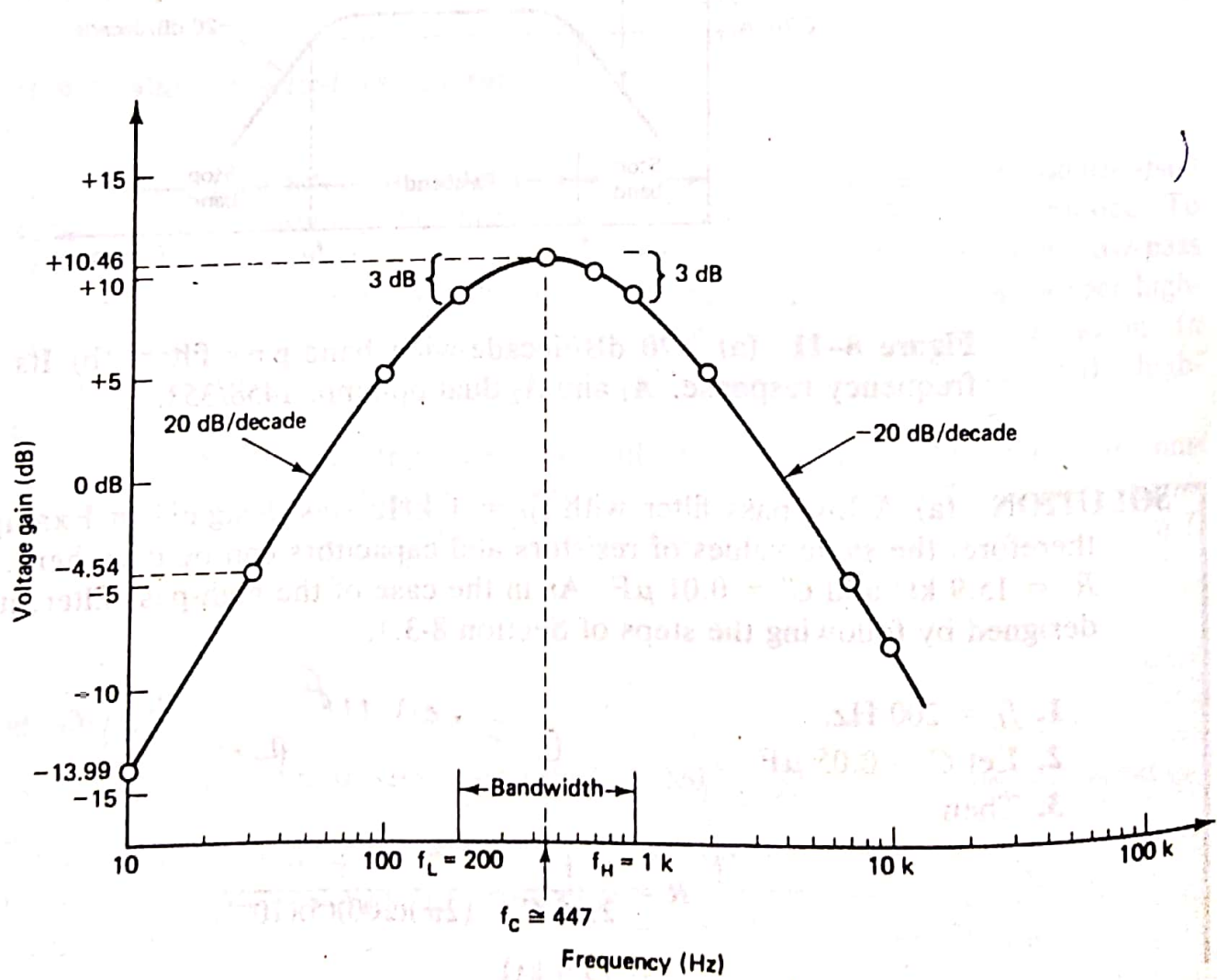


Figure 8-12 Frequency response for Example 8-7.

Substituting this value in Equation (8-9a),

$$Q = \frac{447.2}{1000 - 200} = 0.56$$

Thus Q is less than 10, as expected for the wide band-pass filter.

TABLE 8-5 FREQUENCY RESPONSE DATA FOR THE BAND-PASS FILTER OF EXAMPLE 8-7

Input frequency, $f(\text{Hz})$	Gain magnitude, $ v_o/v_{in} $	Magnitude (dB) = $20 \log v_o/v_{in} $
10	0.1997	-13.99
30	0.5931	-4.54
100	1.780	5.01
200	2.774	8.861
447.2	3.33	10.46
700	3.151	9.969
1,000	2.774	8.861
2,000	1.780	5.001
7,000	0.5655	-4.95
10,000	0.3979	-8.004

* * 8-8.2 Narrow Band-Pass Filter

The narrow band-pass filter using multiple feedback is shown in Figure 8-13. As shown in this figure, the filter uses only one op-amp. Compared to all the filters discussed so far, this filter is unique in the following respects:

1. It has two feedback paths, hence the name *multiple-feedback filter*.
2. The op-amp is used in the *inverting mode*.

Generally, the narrow band-pass filter is designed for specific values of center frequency f_c and Q or f_c and bandwidth [see Equation (8-9a)]. The circuit components are determined from the following relationships.

To simplify the design calculations, choose $C_1 = C_2 = C$.

$$R_1 = \frac{Q}{2\pi f_c C A_F} \quad (8-11)$$

$$R_2 = \frac{Q}{2\pi f_c C (2Q^2 - A_F)} \quad (8-12)$$

$$R_3 = \frac{Q}{\pi f_c C} \quad (8-13)$$

where A_F is the gain at f_c , given by

$$A_F = \frac{R_3}{2R_1} \quad (8-14a)$$

The gain A_F , however, must satisfy the condition

$$A_F < 2Q^2 \quad (8-14b)$$



Another advantage of the multiple feedback filter of Figure 8-13 is that its center frequency f_C can be changed to a new frequency f'_C without changing the gain or bandwidth. This is accomplished simply by changing R_2 to R'_2 so that

$$R'_2 = R_2 \left(\frac{f_C}{f'_C} \right)^2 \quad (8-15)$$

(see Example 8-8).

EXAMPLE 8-8

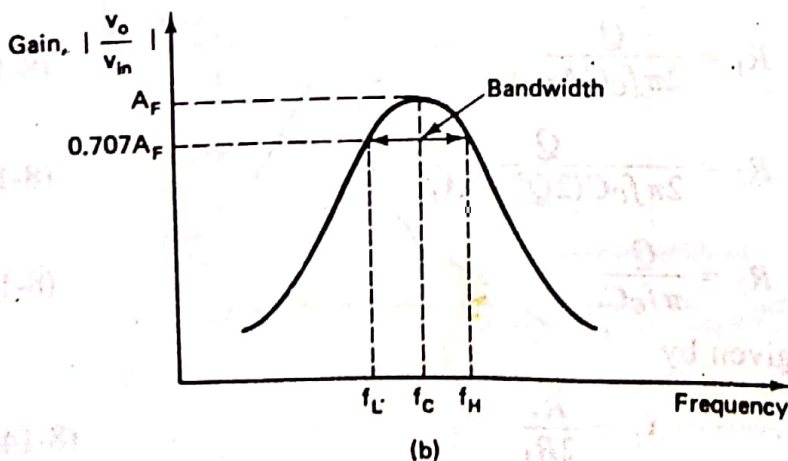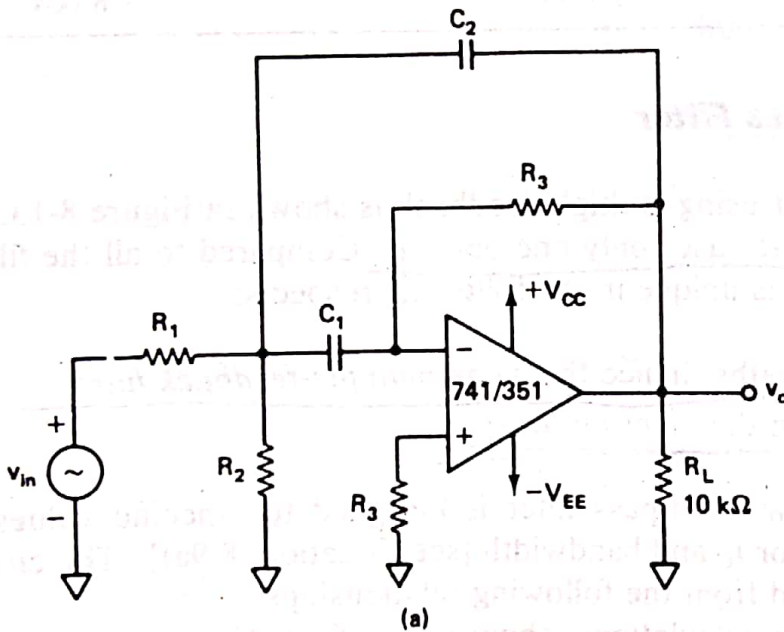- (a) Design the bandpass filter shown in Figure 8-13(a) so that $f_C = 1$ kHz, $Q = 3$, and $A_F = 10$.
 (b) Change the center frequency to 1.5 kHz, keeping A_F and the bandwidth constant.



Handwritten notes:
 $Q = 3$
 $2Q^2 = 10$
 $\Rightarrow 18$
 $10 < 18$
PP2202

Figure 8-13 (a) Multiple-feedback narrow band-pass filter. (b) Its frequency response.

SOLUTION

(a) Choose the values of C_1 and C_2 first and then calculate the values of R_1 , R_2 , and R_3 from Equations (8-11) through (8-13). Let $C_1 = C_2 = C = 0.01 \mu\text{F}$.

$$R_1 = \frac{3}{(2\pi)(10^3)(10^{-8})(10)} = 4.77 \text{ k}\Omega$$

$$R_2 = \frac{3}{(2\pi)(10^3)(10^{-8})[2(3)^2 - 10]} = 5.97 \text{ k}\Omega$$

$$R_3 = \frac{3}{(\pi)(10^3)(10^{-8})} = 95.5 \text{ k}\Omega$$

Use $R_1 = 4.7 \text{ k}\Omega$, $R_2 = 6.2 \text{ k}\Omega$, and $R_3 = 100 \text{ k}\Omega$.

(b) Using Equation (8-15), the value of R'_2 required to change the center frequency from 1 kHz to 1.5 kHz is

$$R'_2 = (5.97 \text{ k}\Omega) \left(\frac{1 \text{ k}}{1.5 \text{ k}} \right)^2 = 2.65 \text{ k}\Omega$$

(Use $R'_2 = 2.7 \text{ k}\Omega$.)

8-9 BAND-REJECT FILTERS

The band-reject filter is also called a *band-stop* or *band-elimination* filter. In this filter, frequencies are attenuated in the stopband while they are passed outside this band, as shown in Figure 8-1(d). As with band-pass filters, the band-reject filters can also be classified as (1) wide band-reject or (2) narrow band-reject. The narrow band-reject filter is commonly called the *notch filter*. Because of its higher Q (>10), the bandwidth of the narrow band-reject filter is much smaller than that of the wide band-reject filter.

8-9.1 Wide Band-Reject Filter $\rightarrow f_L > f_H$

Figure 8-14(a) shows a wide band-reject filter using a low-pass filter, a high-pass filter, and a summing amplifier. To realize a band-reject response, the low cutoff frequency f_L of the high-pass filter must be larger than the high cutoff frequency f_H of the low-pass filter. In addition, the passband gain of both the high-pass and low-pass sections must be equal (see Example 8-9). The frequency response of the wide band-reject filter is shown in Figure 8-14(b).

EXAMPLE 8-9

Design a wide band-reject filter having $f_H = 200 \text{ Hz}$ and $f_L = 1 \text{ kHz}$.

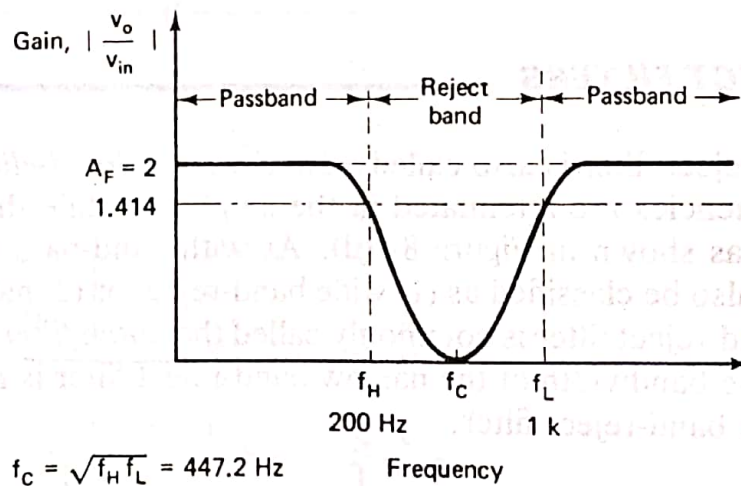
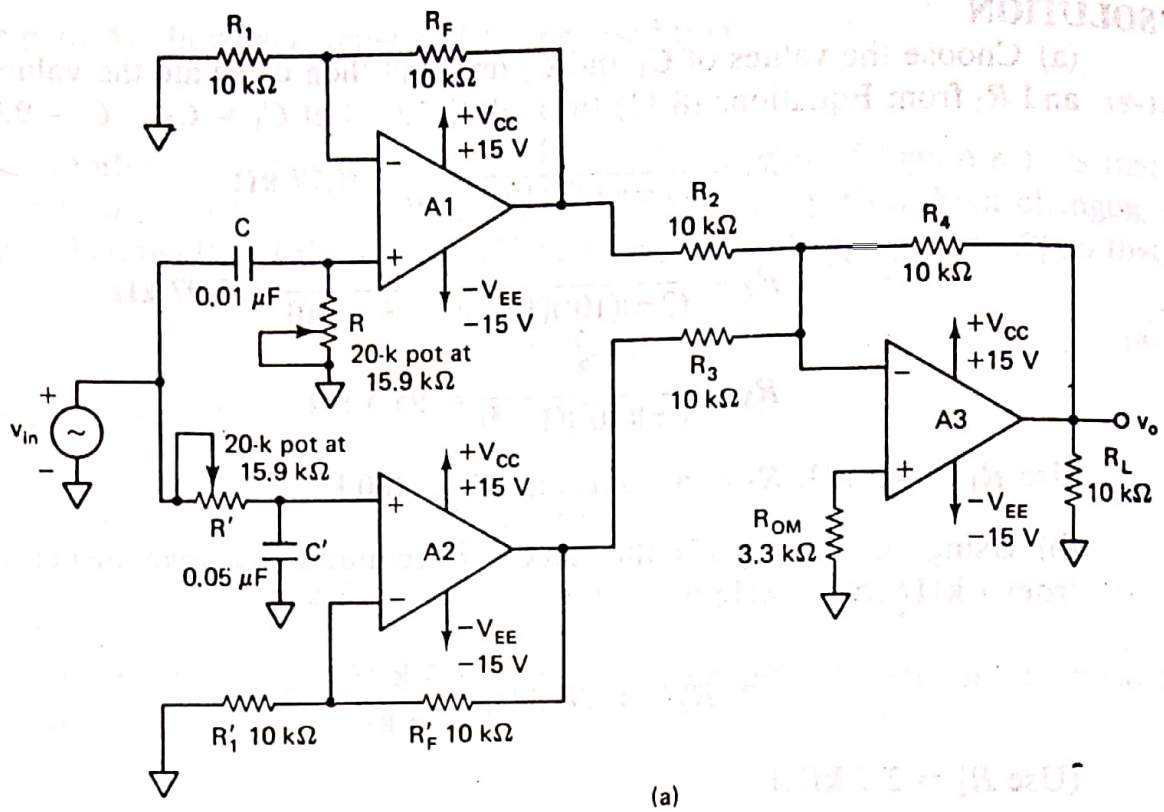


Figure 8-14 Wide band-reject filter. (a) Circuit. (b) Frequency response. For A_1 , A_2 , and A_3 use quad op-amp $\mu\text{AF774}/\text{MC34004}$.

SOLUTION In Example 8-7, a wide band-pass filter was designed with $f_L = 200 \text{ Hz}$ and $f_H = 1 \text{ kHz}$. In this example these band frequencies are interchanged, that is, $f_L = 1 \text{ kHz}$ and $f_H = 200 \text{ Hz}$. This means that we can use the same components as in Example 8-7, but interchanged between high-pass and low-pass sections. Therefore, for the low-pass section, $R' = 15.9 \text{ k}\Omega$ and $C' = 0.05 \mu\text{F}$, while for the high-pass section

$$R = 15.9 \text{ k}\Omega \quad \text{and} \quad C = 0.01 \mu\text{F}$$

Since there is no restriction on the passband gain, use a gain of 2 for each section. Hence let

$$R_1 = R_F = R'_1 = R'_F = 10 \text{ k}\Omega$$

Furthermore, the gain of the summing amplifier is set at 1; therefore,

$$R_2 = R_3 = R_4 = 10 \text{ k}\Omega$$

Finally, the value of $R_{OM} = R_2 \parallel R_3 \parallel R_4 \approx 3.3 \text{ k}\Omega$.

The complete circuit is shown in Figure 8-14(a), and its response is shown in Figure 8-14(b). The voltage gain changes at the rate of 20 dB/decade above f_H and below f_L , with a maximum attenuation occurring at f_C .

8-9.2 Narrow Band-Reject Filter

The narrow band-reject filter, often called the *notch filter*, is commonly used for the rejection of a single frequency such as the 60-Hz power line frequency hum. The most commonly used notch filter is the *twin-T* network shown in Figure 8-15(a). This is a *passive filter* composed of two T-shaped networks. One T network is made up of two resistors and a capacitor, while the other uses two capacitors and a resistor. The *notch-out* frequency is the frequency at which maximum attenuation occurs; it is given by

$$f_N = \frac{1}{2\pi RC} \quad (8-16)$$

Unfortunately, the passive twin-T network has a relatively low figure of merit Q . The Q of the network can be increased significantly if it is used with the voltage follower as shown in Figure 8-15(b). The frequency response of the active notch filter of Figure 8-15(b) is shown in Figure 8-15(c). The most common use of notch filters is in communications and biomedical instruments for eliminating undesired frequencies. To design an active notch filter for a specific notch-out frequency f_N , choose the value of $C \leq 1 \mu\text{F}$ and then calculate the required value of R from Equation (8-16). For the best response, the circuit components should be very close to their indicated values.


EXAMPLE 8-10

Design a 60-Hz active notch filter.


SOLUTION Let $C = 0.068 \mu\text{F}$. Then, from Equation (8-16), the value of R is

$$R = \frac{1}{2\pi f_N C} = \frac{1}{(2\pi)(60)(68)(10^{-9})} = 39.01 \text{ k}\Omega$$

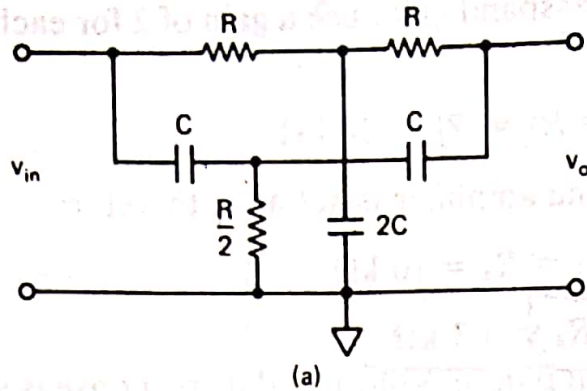
(Use 39 k Ω .) For $R/2$, parallel two 39-k Ω resistors; for the $2C$ component, parallel two 0.068- μF capacitors.



(a)

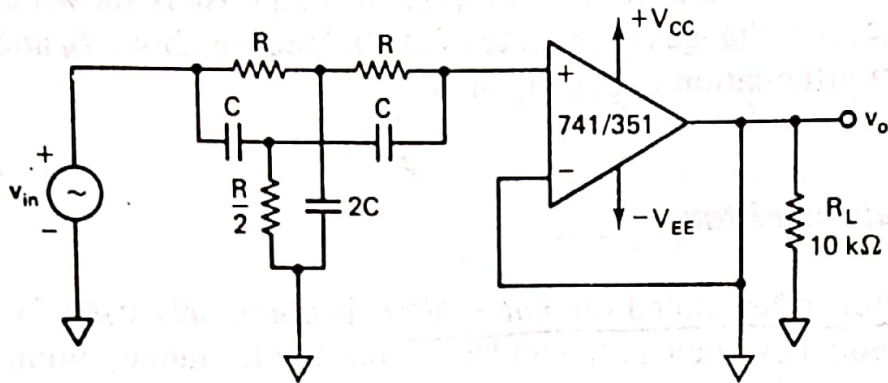

(b)

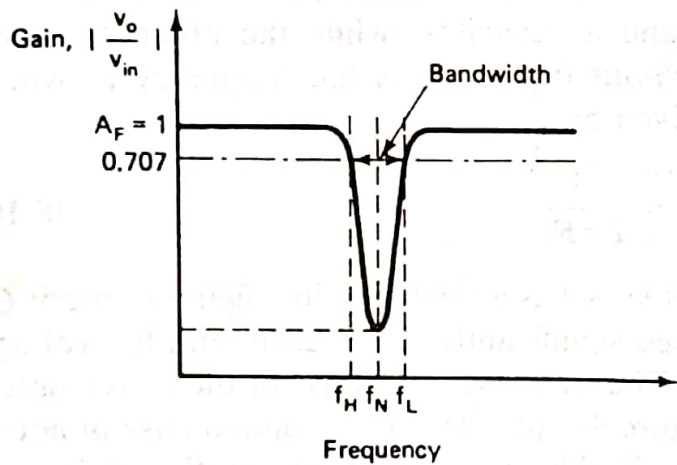

(c)


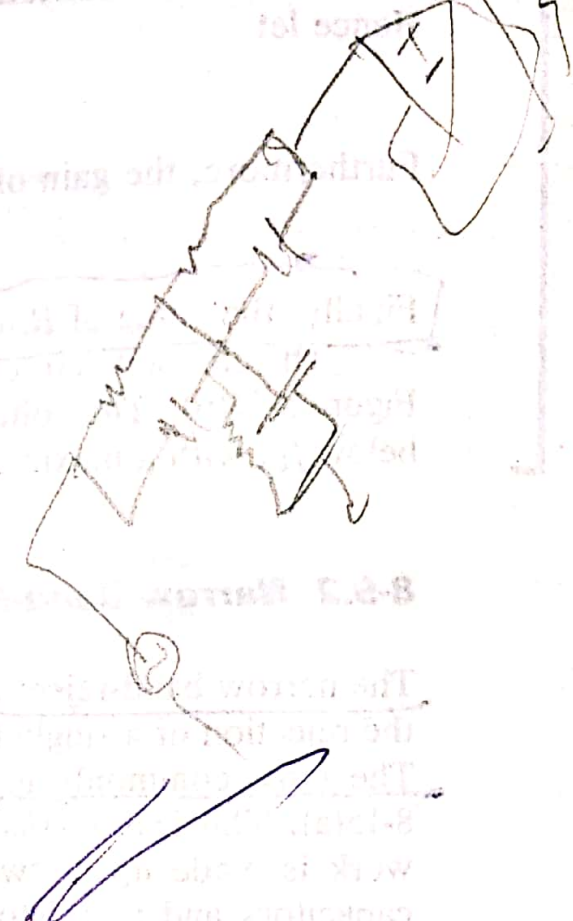


Figure 8-15 (a) Twin-T notch filter. (b) Active notch filter. (c) Frequency response of the active notch filter.

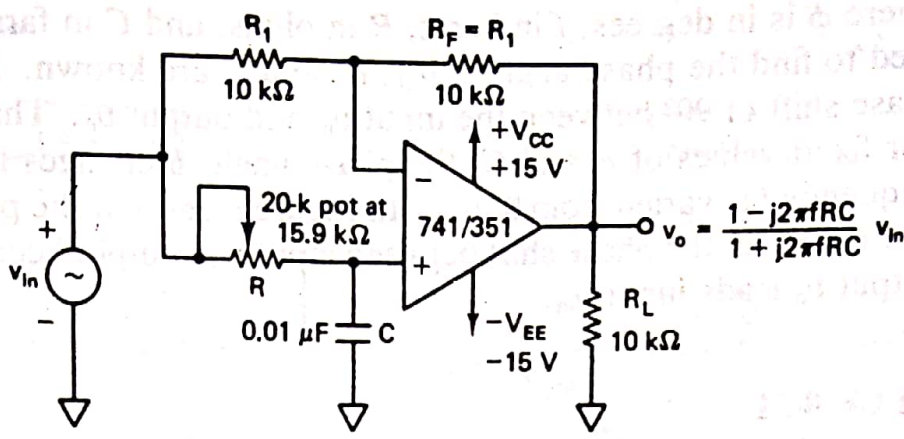
8-10 ALL-PASS FILTER

As the name suggests, an all-pass filter passes all frequency components of the input signal without attenuation, while providing predictable phase shifts for different frequencies of the input signal. When signals are transmitted over transmission lines, such as telephone wires, they undergo change in phase. To compensate for these phase changes, all-pass filters are required. The all-pass filters are also called *delay equalizers* or *phase correctors*. Figure 8-16(a) shows an all-pass filter wherein $R_F = R_1$. The output voltage v_o of the filter can be obtained by using the superposition theorem:

$$v_o = -v_{in} + \frac{-jX_C}{R - jX_C} v_{in(2)} \quad (8-17)$$



(a)

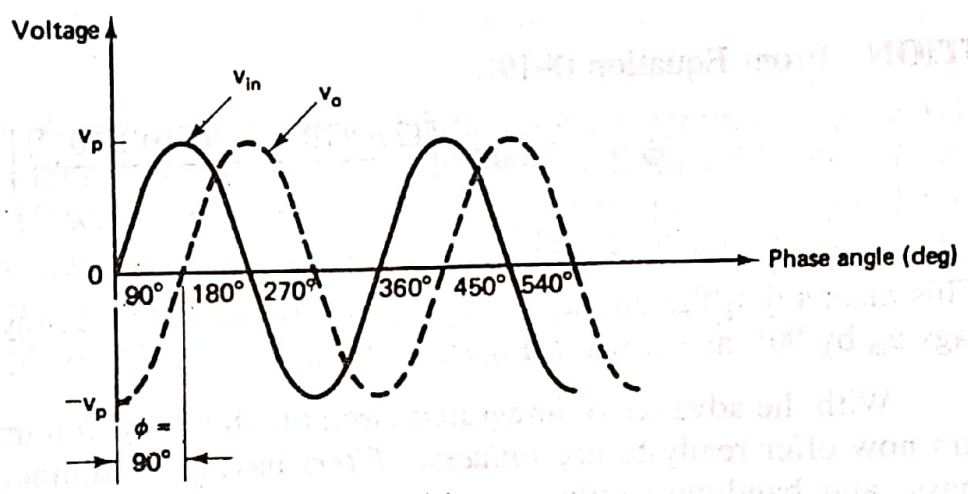

(b)

Figure 8-16 All-pass filter. (a) Circuit. (b) Phase shift between input and output voltages.

But $-j = 1/j$ and $X_C = 1/2\pi fC$. Therefore, substituting for X_C and simplifying, we get

$$v_o = v_{in} \left(-1 + \frac{2}{j2\pi fRC + 1} \right)$$

or

$$\frac{v_o}{v_{in}} = \frac{1 - j2\pi fRC}{1 + j2\pi fRC} \tag{8-18}$$

where f is the frequency of the input signal in hertz.

Equation (8-18) indicates that the amplitude of v_o/v_{in} is unity; that is, $|v_o| = |v_{in}|$ throughout the useful frequency range, and the phase shift between v_o and v_{in} is a function of input frequency f . The phase angle ϕ is given by

$$\phi = -2 \tan^{-1} \left(\frac{2\pi fRC}{1} \right) \tag{8-19}$$

where ϕ is in degrees, f in hertz, R in ohms, and C in farads. Equation (8-19) is used to find the phase angle ϕ if f , R , and C are known. Figure 8-16(b) shows a phase shift of 90° between the input v_{in} and output v_o . That is, v_o lags v_{in} by 90° . For fixed values of R and C , the phase angle ϕ changes from 0 to -180° as the frequency f is varied from 0 to ∞ . In Figure 8-16(a), if the positions of R and C are interchanged, the phase shift between input and output becomes positive. That is, output v_o leads input v_{in} .

EXAMPLE 8-11

For the all-pass filter of Figure 8-16(a), find the phase angle ϕ if the frequency of v_{in} is 1 kHz.

SOLUTION From Equation (8-19),

$$\begin{aligned}\phi &= -2 \tan^{-1} \left[\frac{(2\pi)(10^3)(15.9)(10^3)(10^{-8})}{1} \right] \\ &= -90^\circ\end{aligned}$$

This means that the output voltage v_o has the same frequency and amplitude but lags v_{in} by 90° , as shown in Figure 8-16(b).

With the advance of integrated-circuit technology, a number of manufacturers now offer ready-to-use *universal filters* having simultaneous low-pass, high-pass, and band-pass output responses. Notch and all-pass functions are also available by combining these output responses in the uncommitted op-amp. Because of its versatility, this filter is called the *universal filter*. It provides the user with easy control of the gain and Q factor. The universal filter, sometimes called a *state-variable filter*, is presented in Chapter 10.